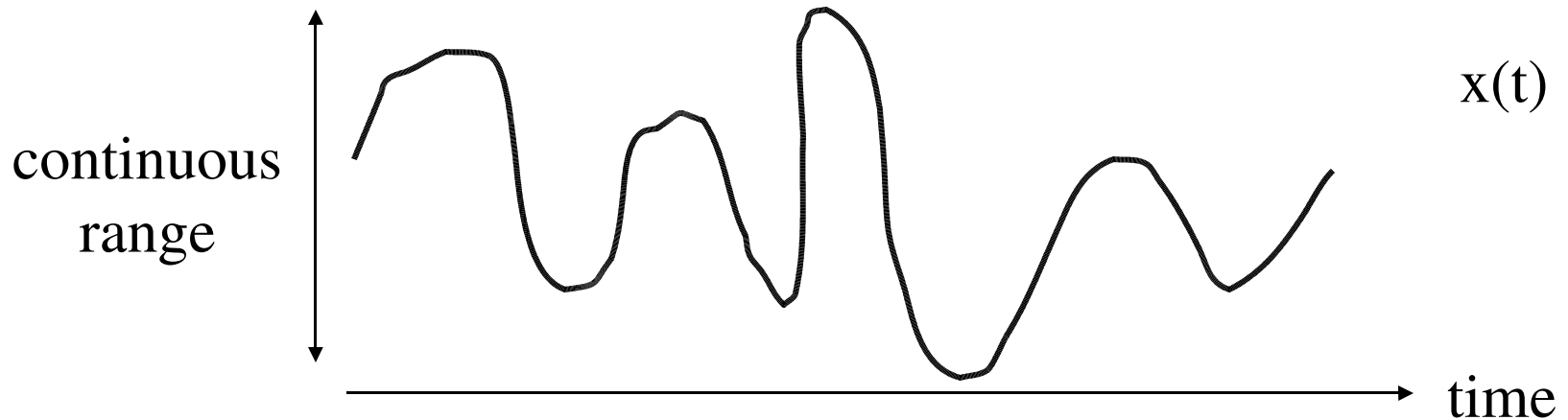


Analog/Digital Conversion

Interfacing a microprocessor-based system to the real world.


- Analog and digital signals
- The bridge: Sampling Theorem
- Conversion concepts
- Conversion circuitry

Analog Signals



- The real world is analog.
- Signals vary continuously with time.
- Analog signals take arbitrarily many values.
- Examples:
 - audio signal from microphone or cassette player
 - video signal from VCR or video camera
 - x/y voltage outputs from joystick

Digital Signals

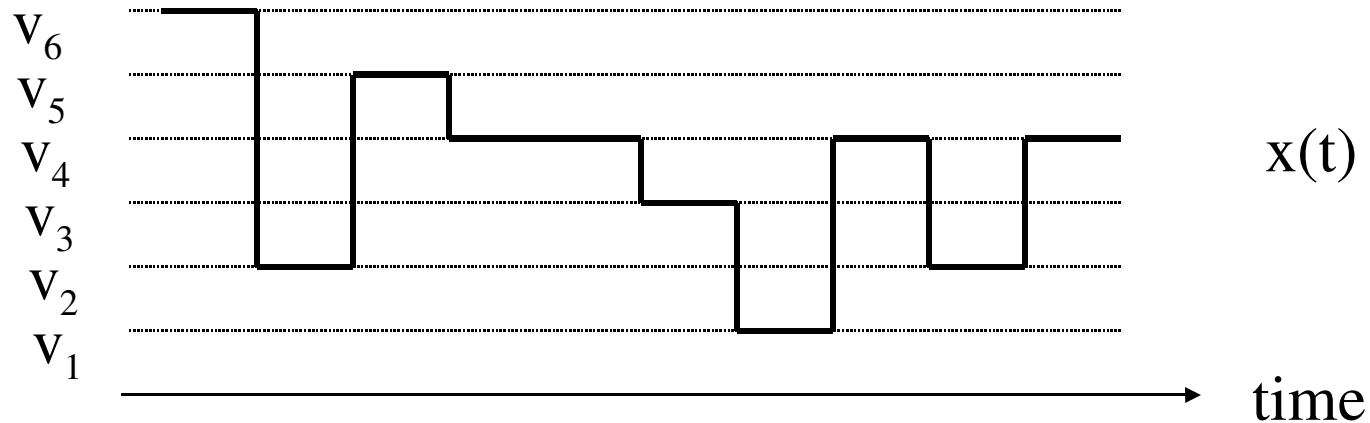


- The microprocessor world is digital.
- Limited number of separate (discrete) values at each time step.
- Digital signals take only these values, nothing inbetween.
- Computers: Two values (0 or 1) corresponding to low/high value of electrical property (usually voltage).
- In general: 2^n values (n-bit representation).

Analog vs. Digital

With digital signals, it is possible to:


Signal Conversion

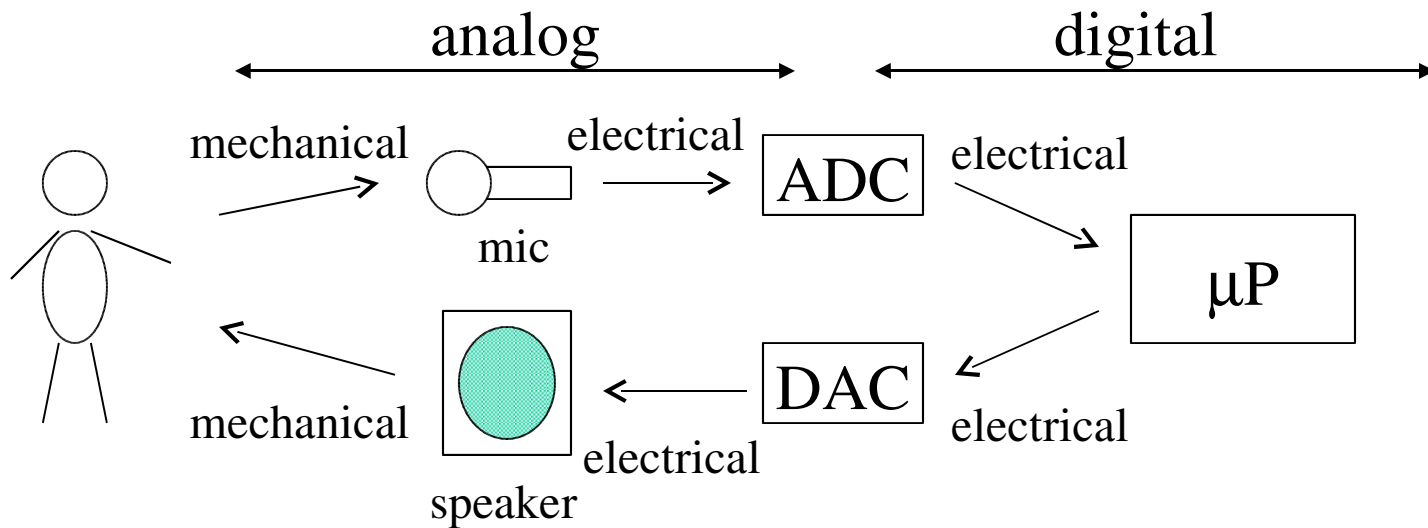- To interface microprocessors to real-world (analog) systems, we need **converters**.
- Digital to Analog Converters (DAC): Convert a digital input (e.g. binary word) to analog output (e.g. current or voltage).
- Analog to Digital Converters (ADC): Convert an analog input to digital output.




Analog to Digital Conversion

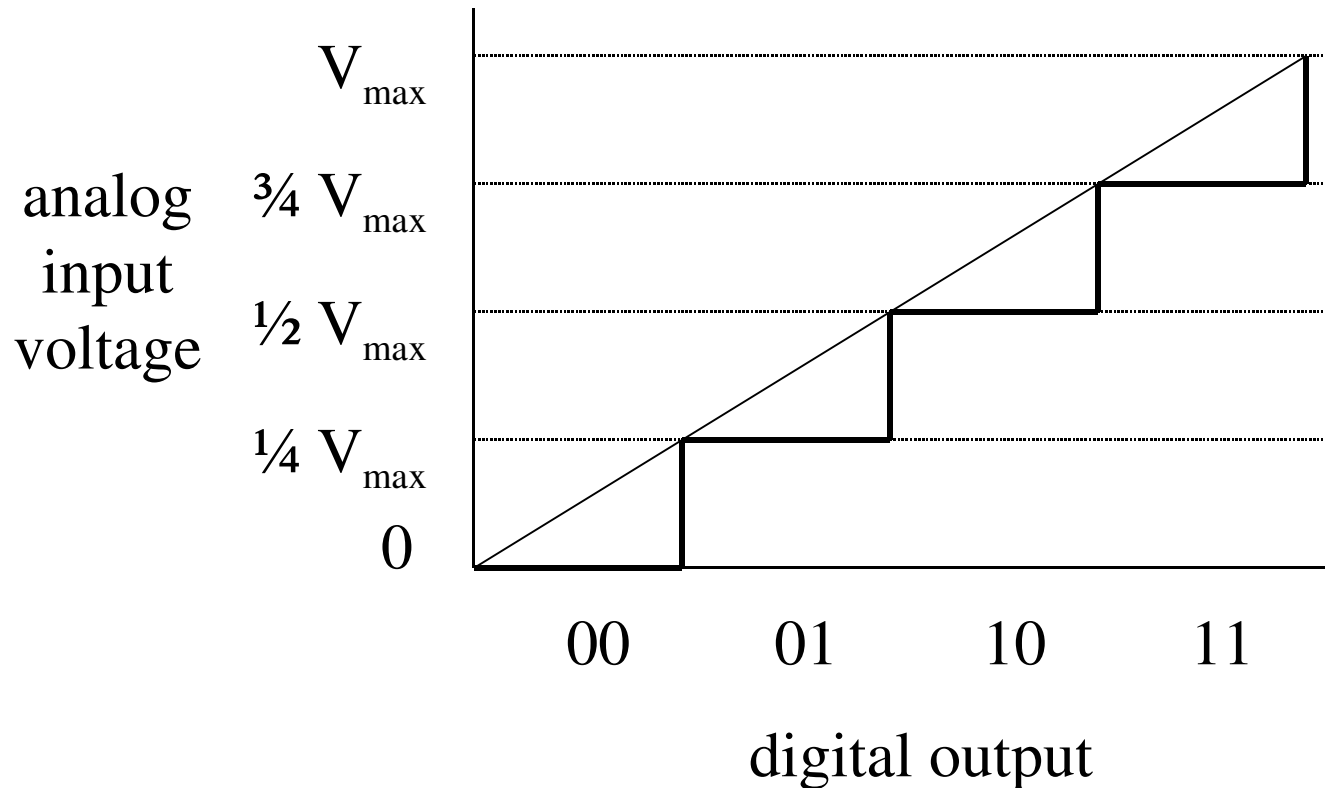
- Ideal 2-bit ADC
- Input range: Analog voltage between 0 and V_{\max}
- Output: 2-bit code



Is this any better?

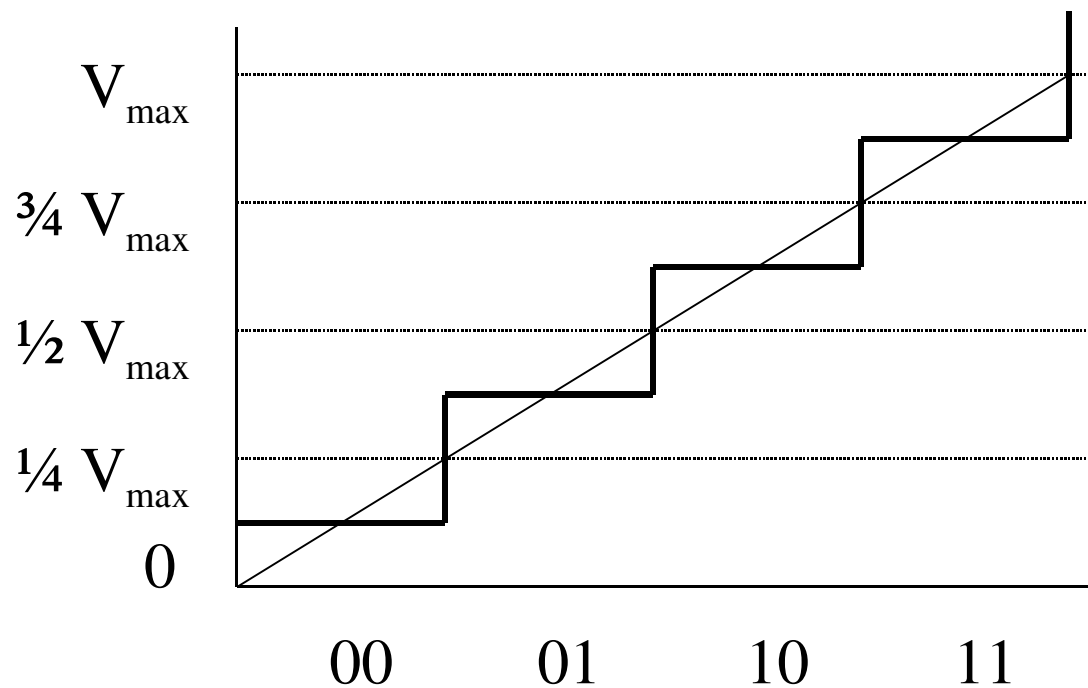


Conversion of Signals over Time

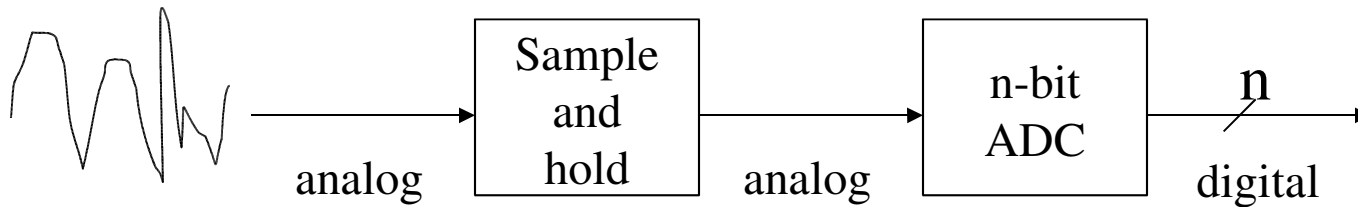


- Must **hold** input signal while converting.
- “Sample and hold” circuit takes in (samples) analog value and holds it still while A to D conversion is taking place.
- What is the minimum rate S at which the analog input should be sampled?
- Minimum sampling rate S determines the minimum acceptable speed of A to D conversion.

Sampling

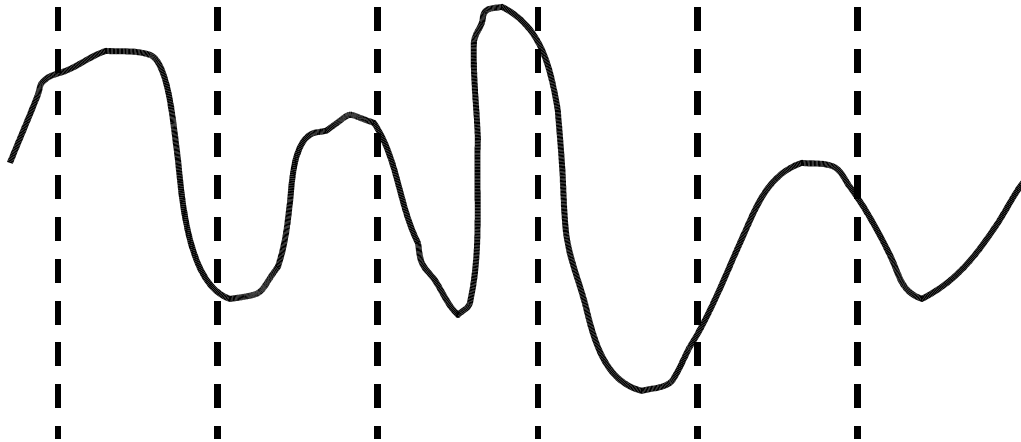


- Sampling rate must be high enough so that “no information is lost”.
- What is the information of a signal?

A Simple Case

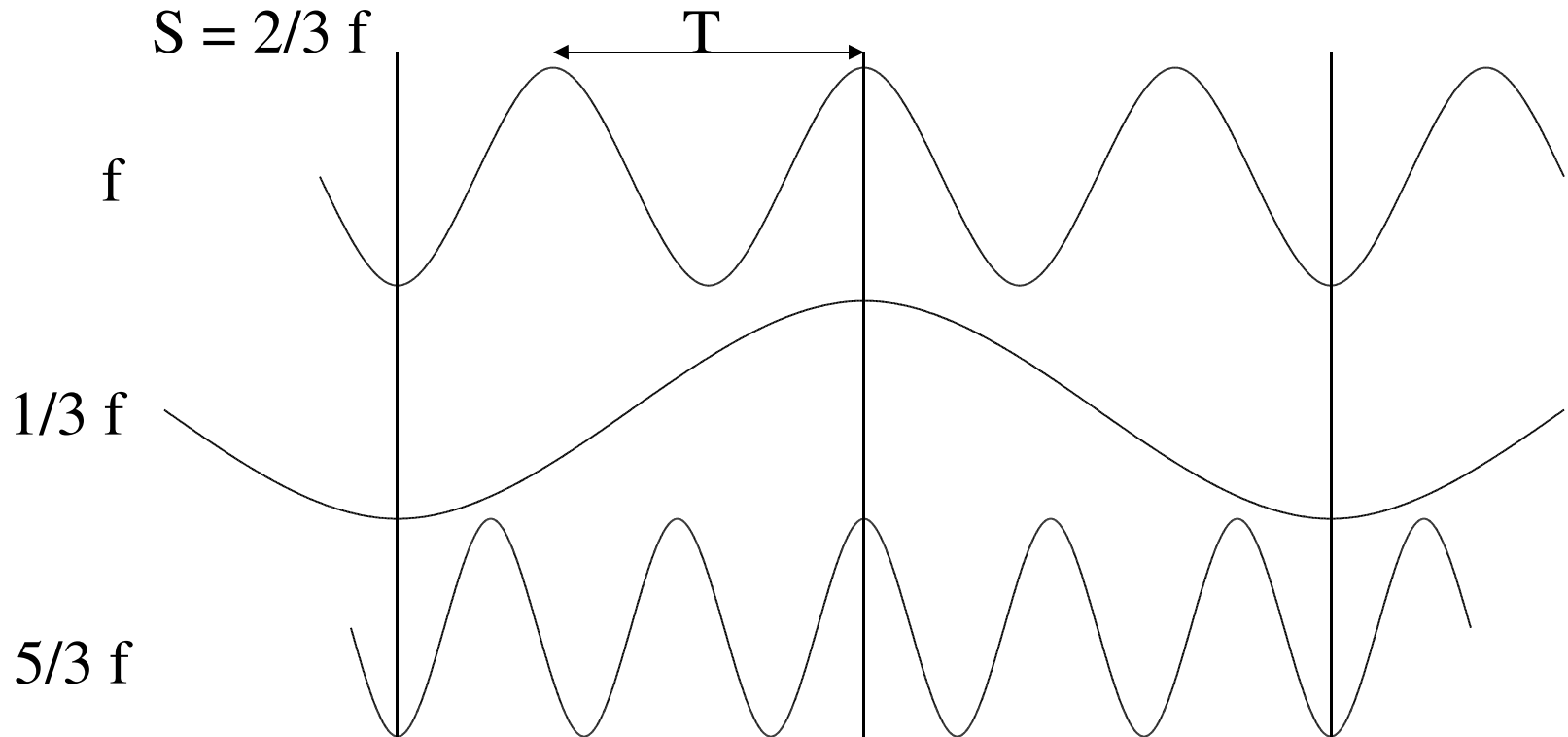


- Detecting a sinusoidal signal of frequency at least $f = 1/T$
- What is the minimum sampling rate required for detection?


Going Faster

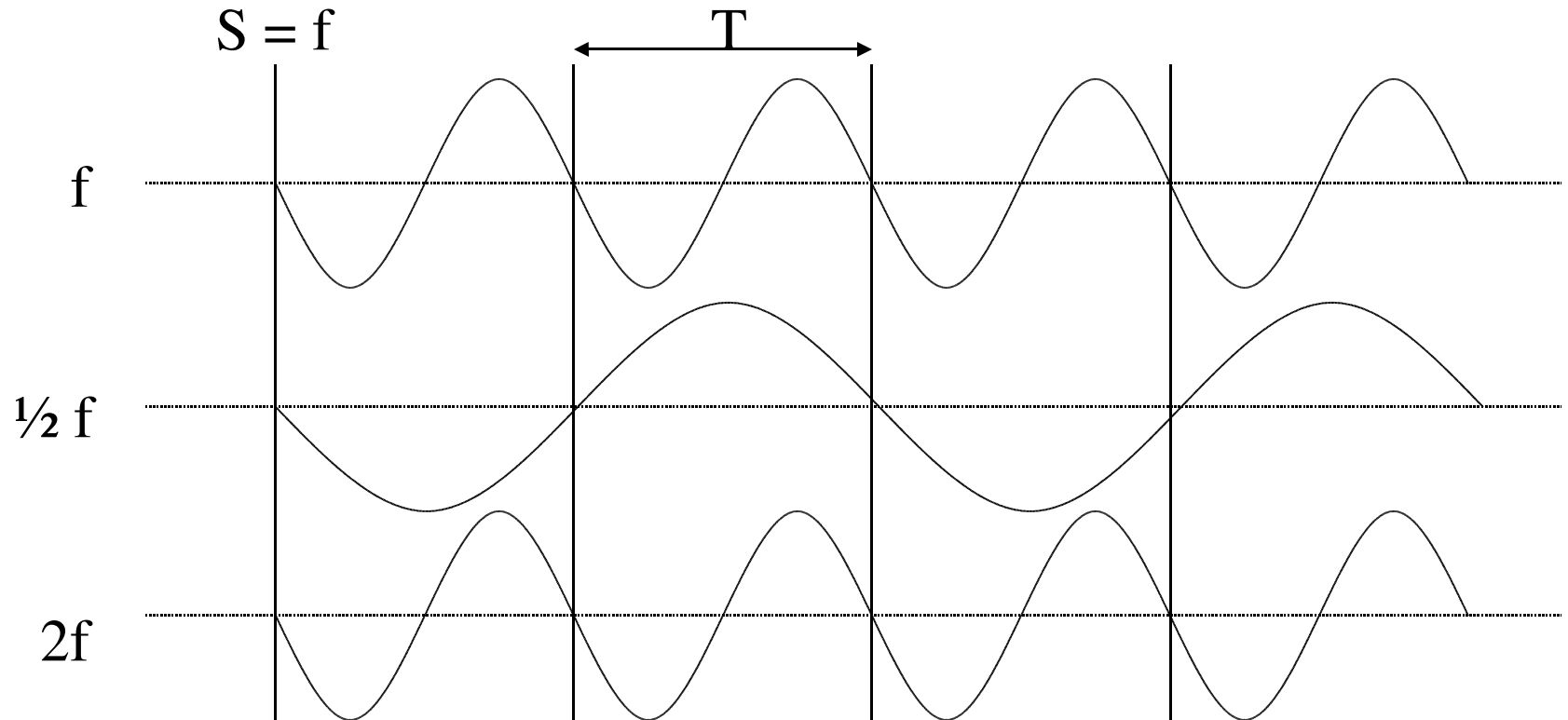

Fast Enough

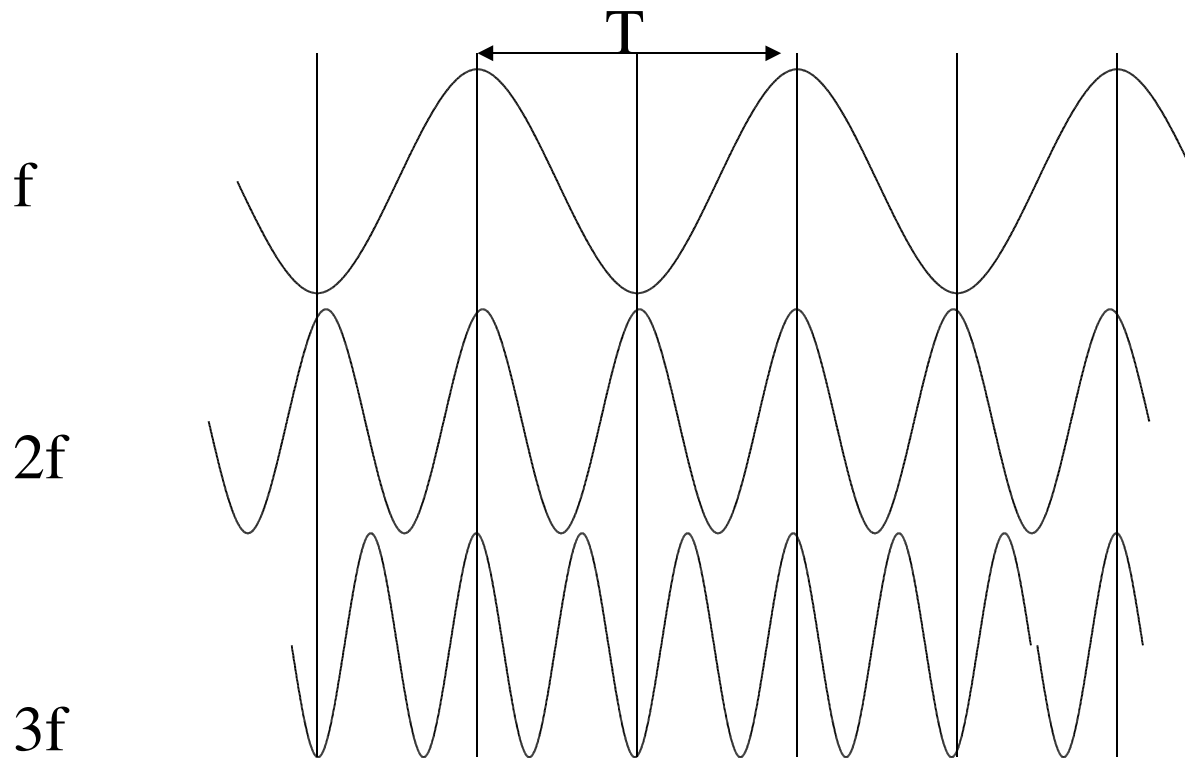

More Than Enough

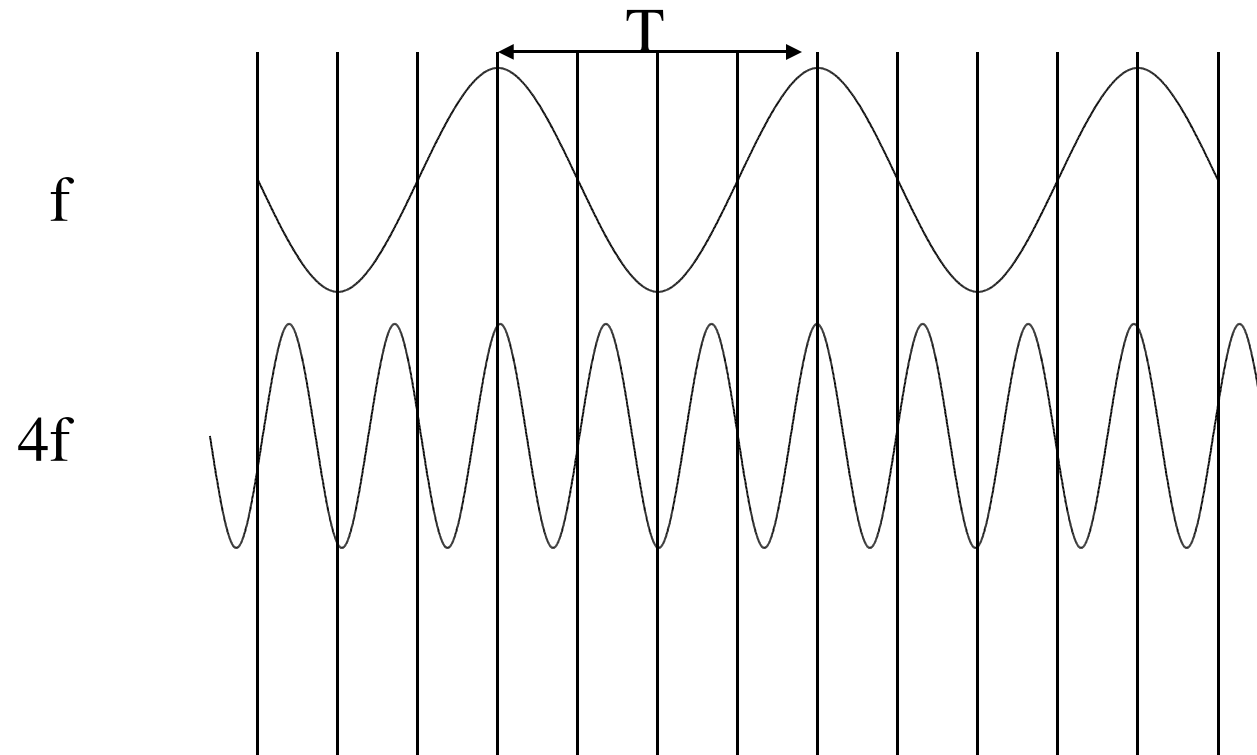

Sampling Theorem

Harmonic analysis

Signals can be expressed as weighted sums of harmonic functions.

Shannon's Theorem (Nyquist Sampling Theorem)

To sample a bandlimited signal $x(t)$ with no loss of information, the sampling rate must be at least twice the frequency of the highest frequency component.

Example: Audio signals typically include components up to 20KHz. CDs sample at 44.1KHz. DATs sample at 32, 44.1, or 48KHz.

Basic Converter Characteristics


Resolution: Fraction of analog range as defined by the number of bits on the digital side of the converter.

- An n-bit ADC divides analog voltage range $[0, V_{\max}]$ into _____ sections and its resolution is _____ of V_{\max} .

Error: Difference between analog value you believe a digital value represents and what that analog value actually is.


- Even ideal converters introduce some error.

Quantization Error

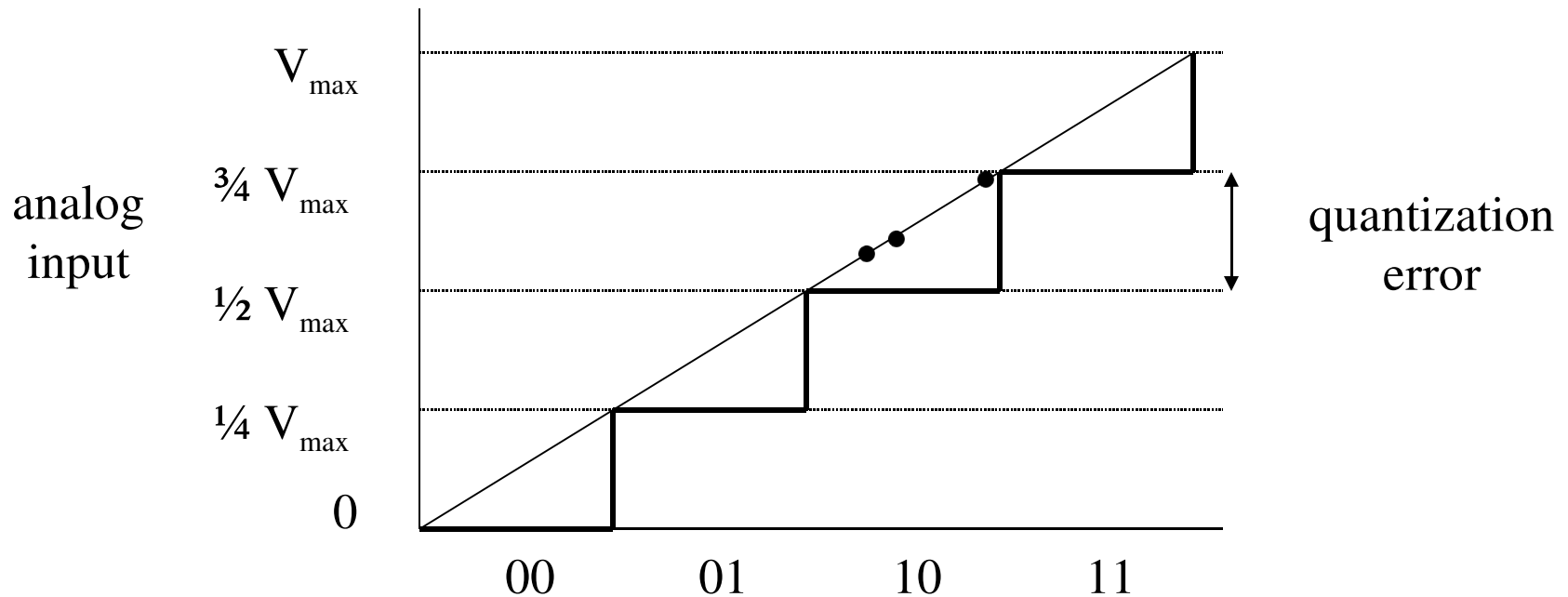

- Inherent in converting continuous values to a finite number of discrete values.
 - Every voltage in the range $[\frac{1}{2} V_{\max}, \frac{3}{4} V_{\max})$ is mapped to “01”.
 - To minimize worst-case error, we assume that “01” means _____ V_{\max} .
 - Worst-case error is _____.
- Absolute error depends on _____ and _____.
- For normalization, quantization error is expressed in terms of the ideal analog difference represented by a unit change in the digital value, referred to as LSB.
- Quantization error is always equal to $\pm \frac{1}{2}$ LSB.

Accuracy

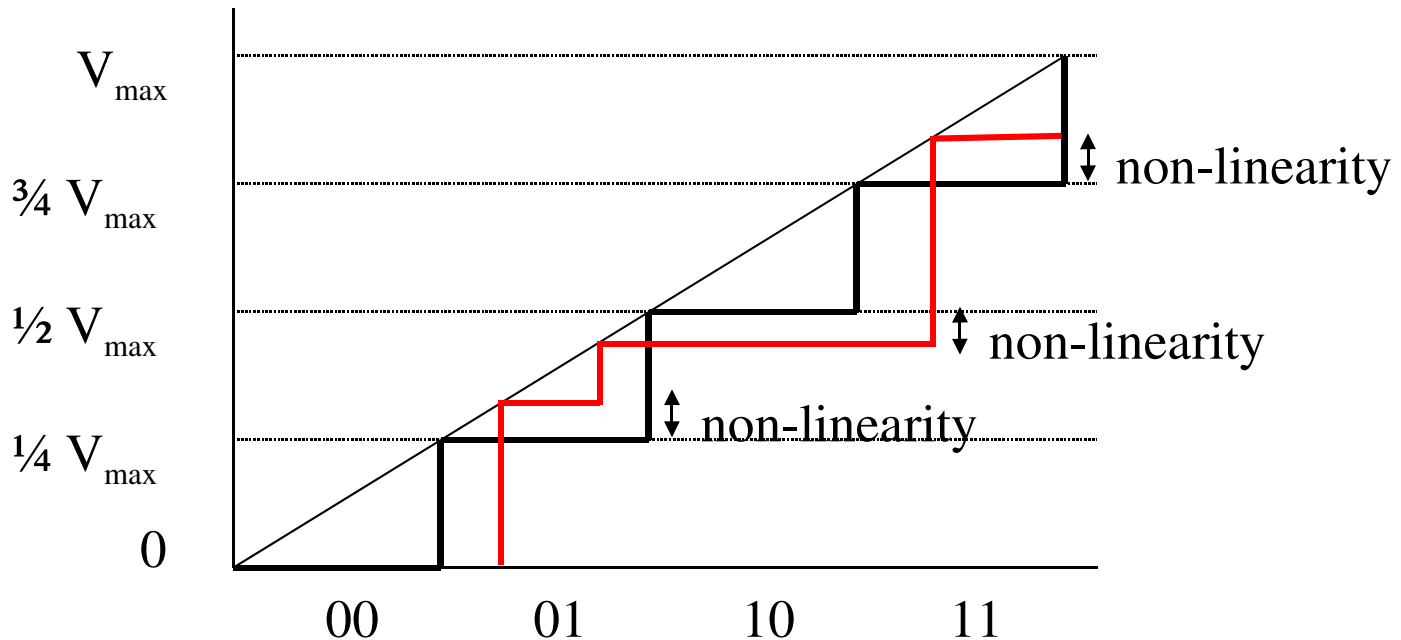

- Absolute non-linearity: Absolute deviation from ideal transfer curve.
- Differential non-linearity: Deviation of the difference between two consecutive codes from ideal 1 LSB. An absolute non-linearity of $\pm \frac{1}{4}$ LSB results in differential non-linearity of $\pm \frac{1}{2}$ LSB.
- What happens if non-linearity exceeds $\pm \frac{1}{2}$ LSB ?

Conversion Time

Amount of time from changing input value to output value becoming stable (typically in the ns to μ s range).


ADCs

- Sample and hold: May (or not) rely on external sample and hold.
- Averaging: Code represents average input over conversion time.
- Typically provide “end of conversion” signal that can be used as an interrupt.
- Trick question: To achieve sampling rate S , what is the maximum acceptable ADC conversion time?

DACs


- Conversion time usually referred to as the settling time required for output to reach specified accuracy.
- Most DACs can be driven faster than specified conversion rate at a corresponding loss of accuracy.

DAC #1: Voltage Divider

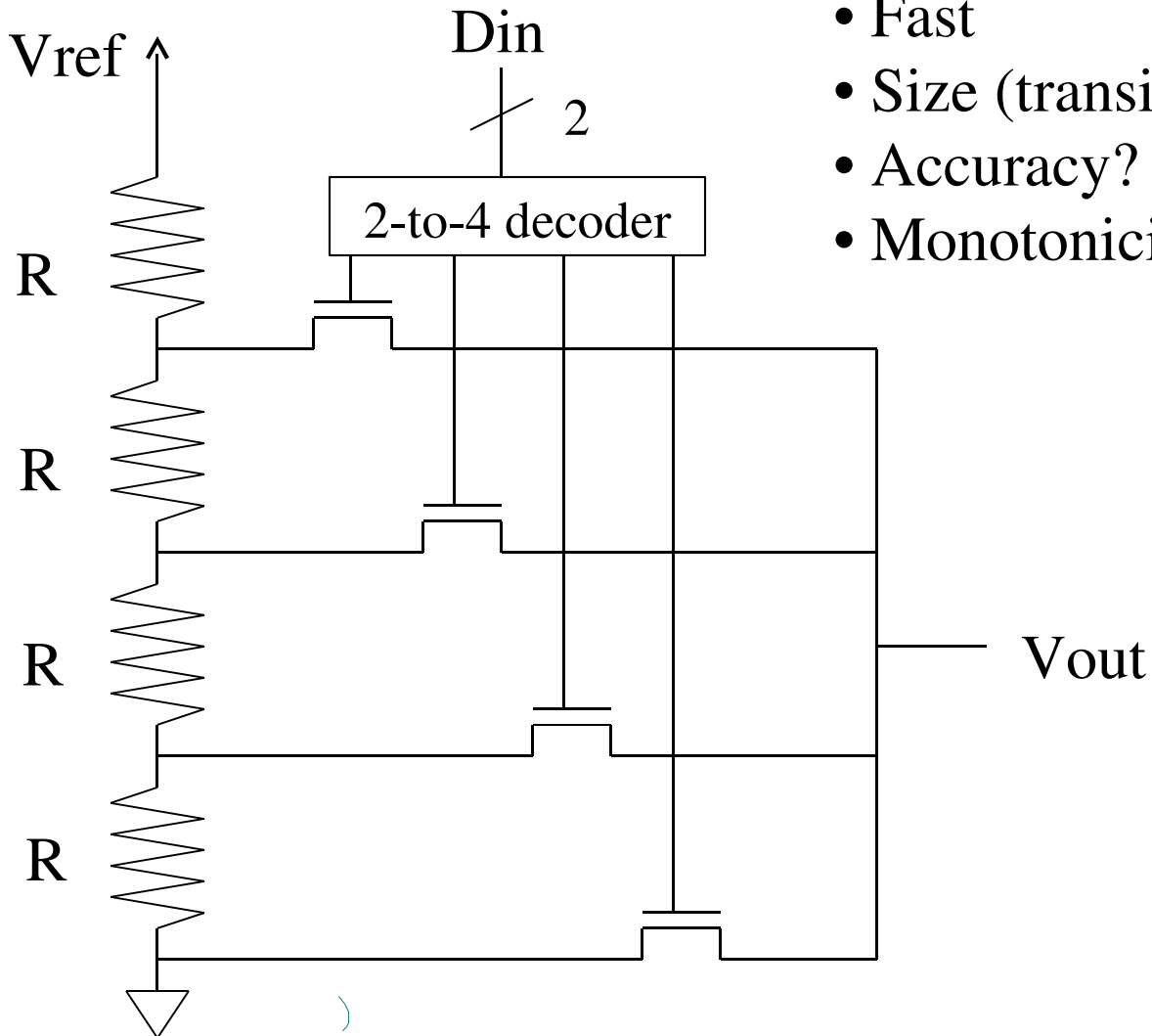


- Fast
- Size (transistors, switches)?
- Accuracy?
- Monotonicity?

DAC #2: R/2R Ladder

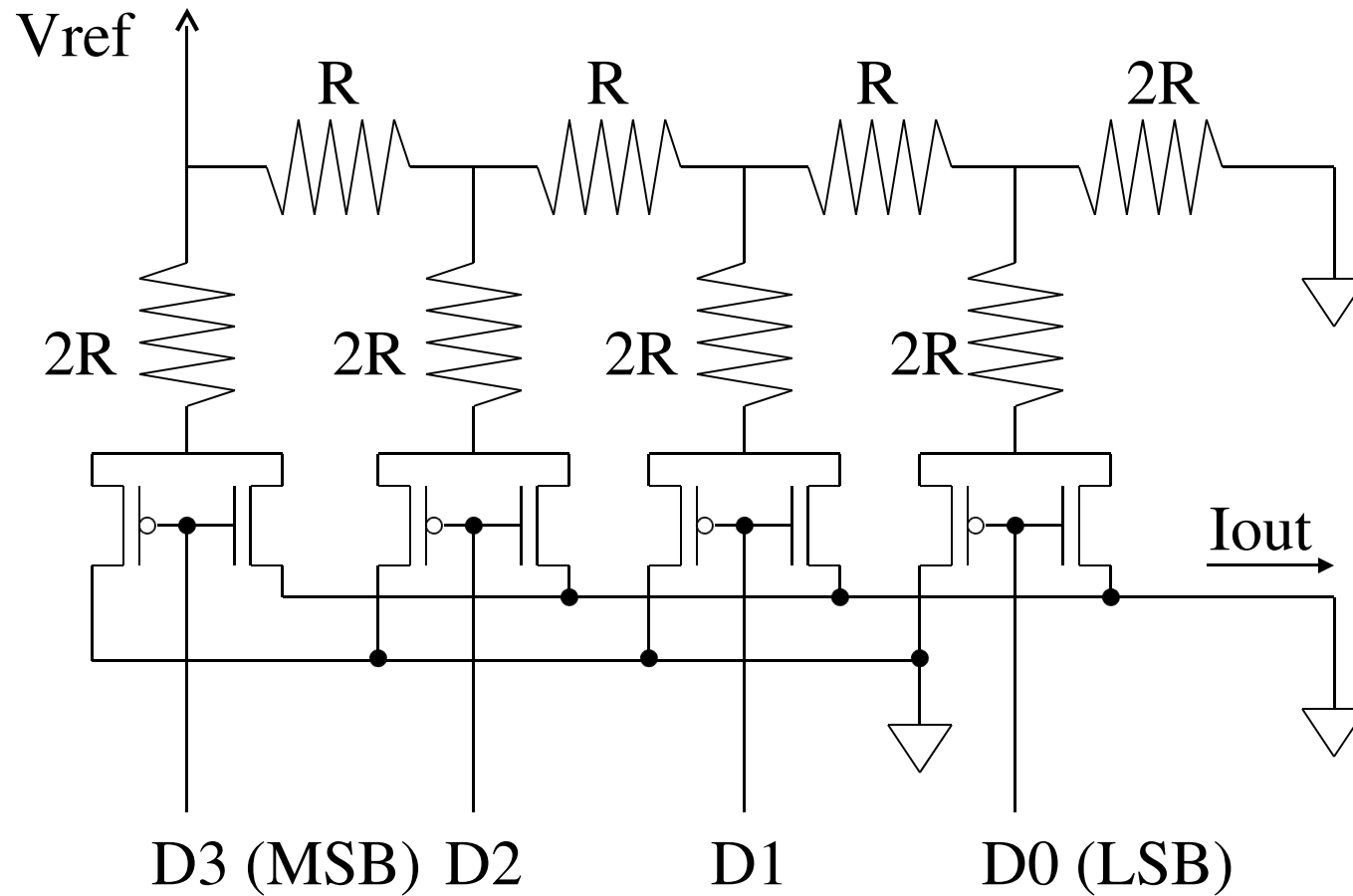


- Size?
- Accuracy?
- Monotonicity? (Consider 0111 \rightarrow 1000)

ADC #1: Flash

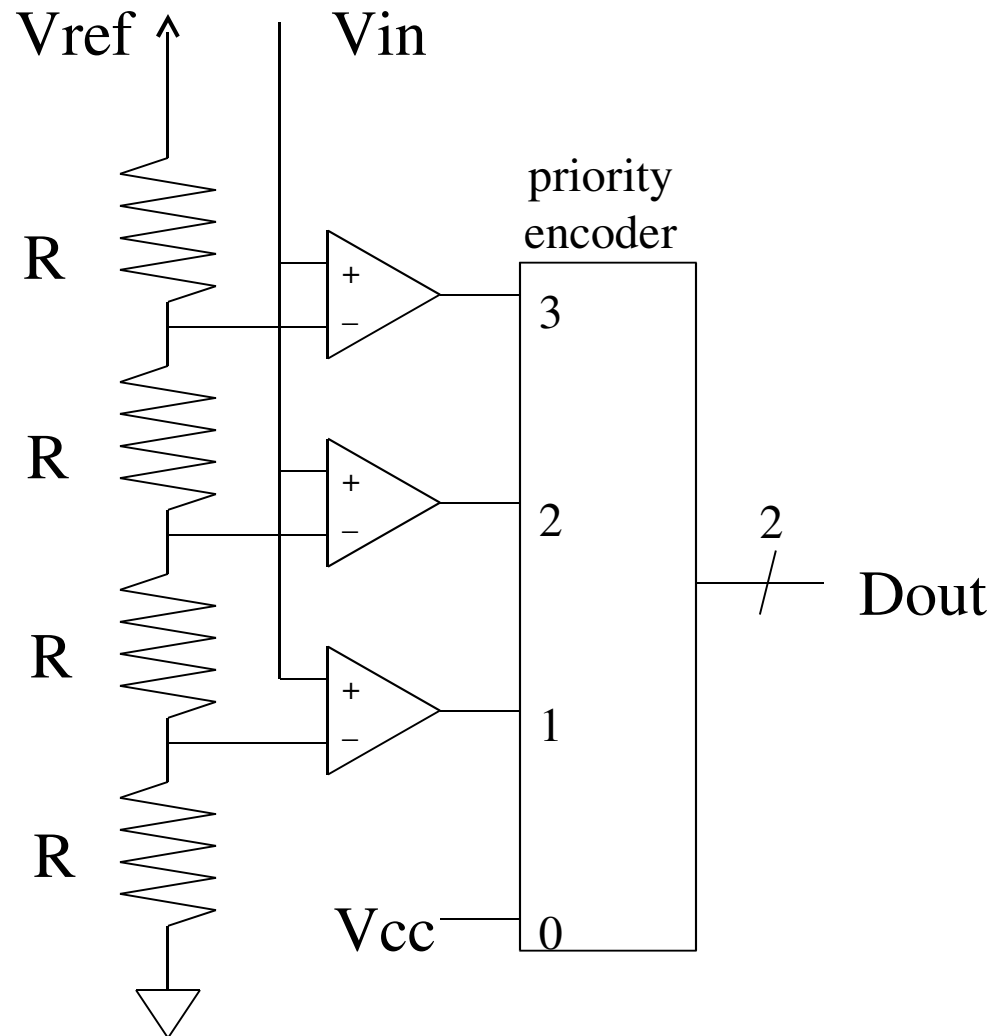


ADC #2: Single-Slope Integration

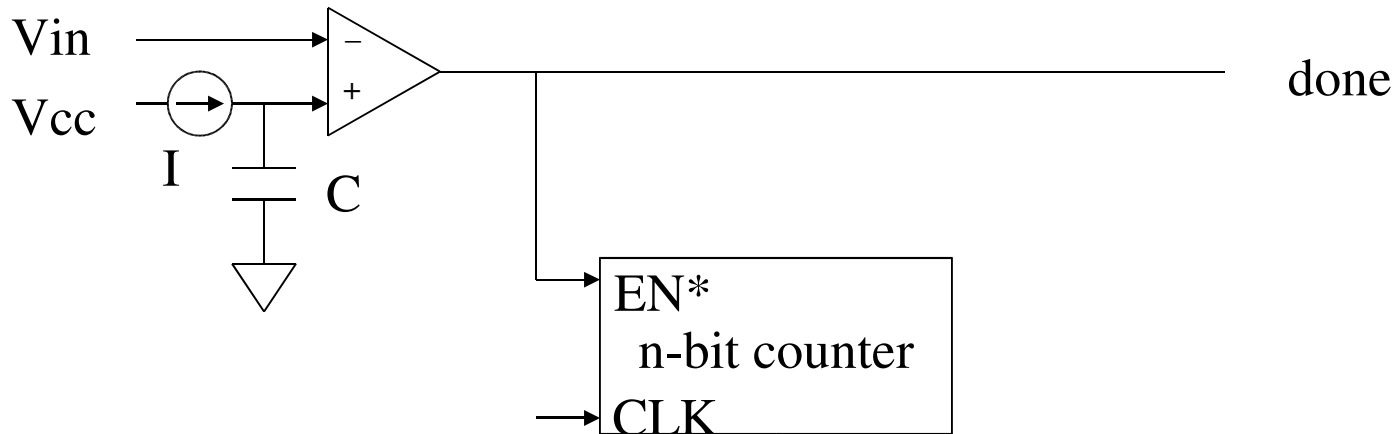

- Start: Reset counter, discharge C.
- Charge C at fixed current I until $V_c > V_{in}$. How should C, I, n, and CLK be related?
- Final counter value is Dout.
- Conversion may take several milliseconds.
- Good differential linearity.
- Absolute linearity depends on precision of C, I, and clock.

ADC #3: Successive Approximation (1/2)

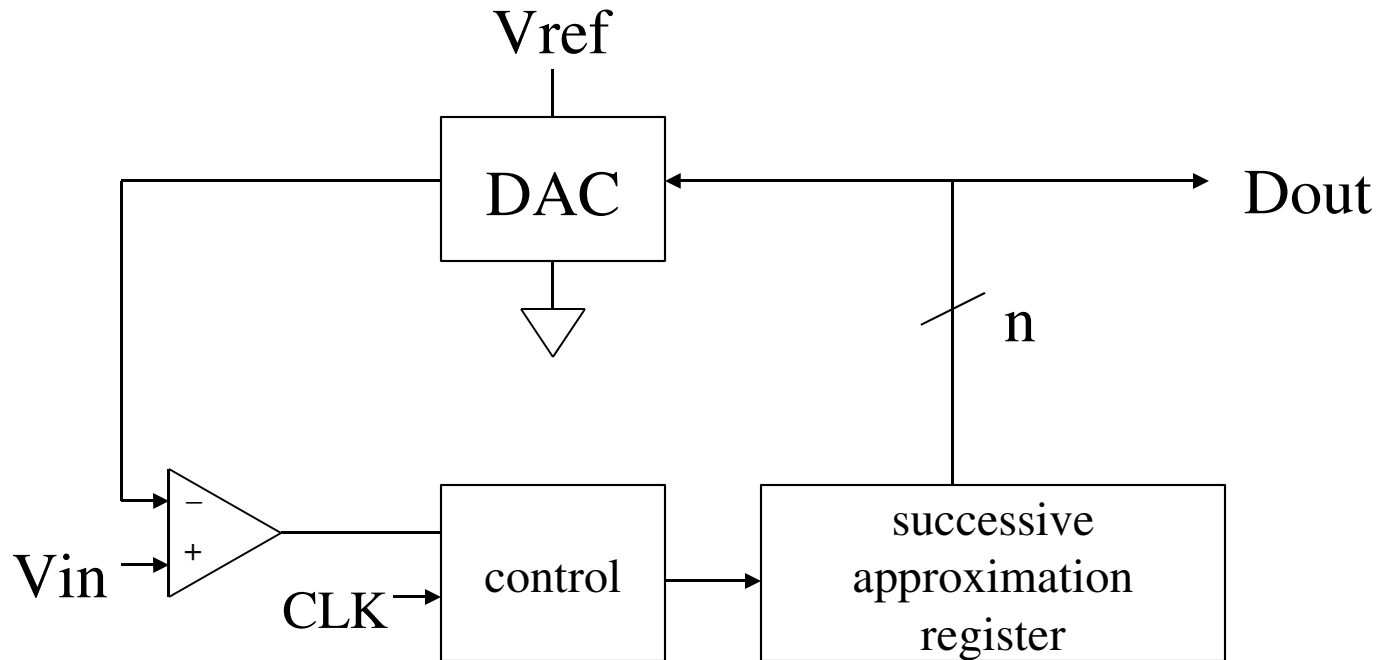

- Binary search to match input voltage.
- Conversion time $> n$ times DAC settling time.
- Input should stay stable throughout conversion.

Successive Approximation Algorithm

Binary search algorithm


0. Set successive approximation register to 0
2. For each bit from MSB to LSB do
 3. flip bit to 1
 3. if DAC output > V_{in} , reset bit to 0

Example

$V_{ref} = 15V$, $V_{in} = 10V$, 4 bits , binary code = voltage value

iteration	DAC out	comparison	$A_3A_2A_1A_0$
-----------	---------	------------	----------------


FIGURE 1. Resistor

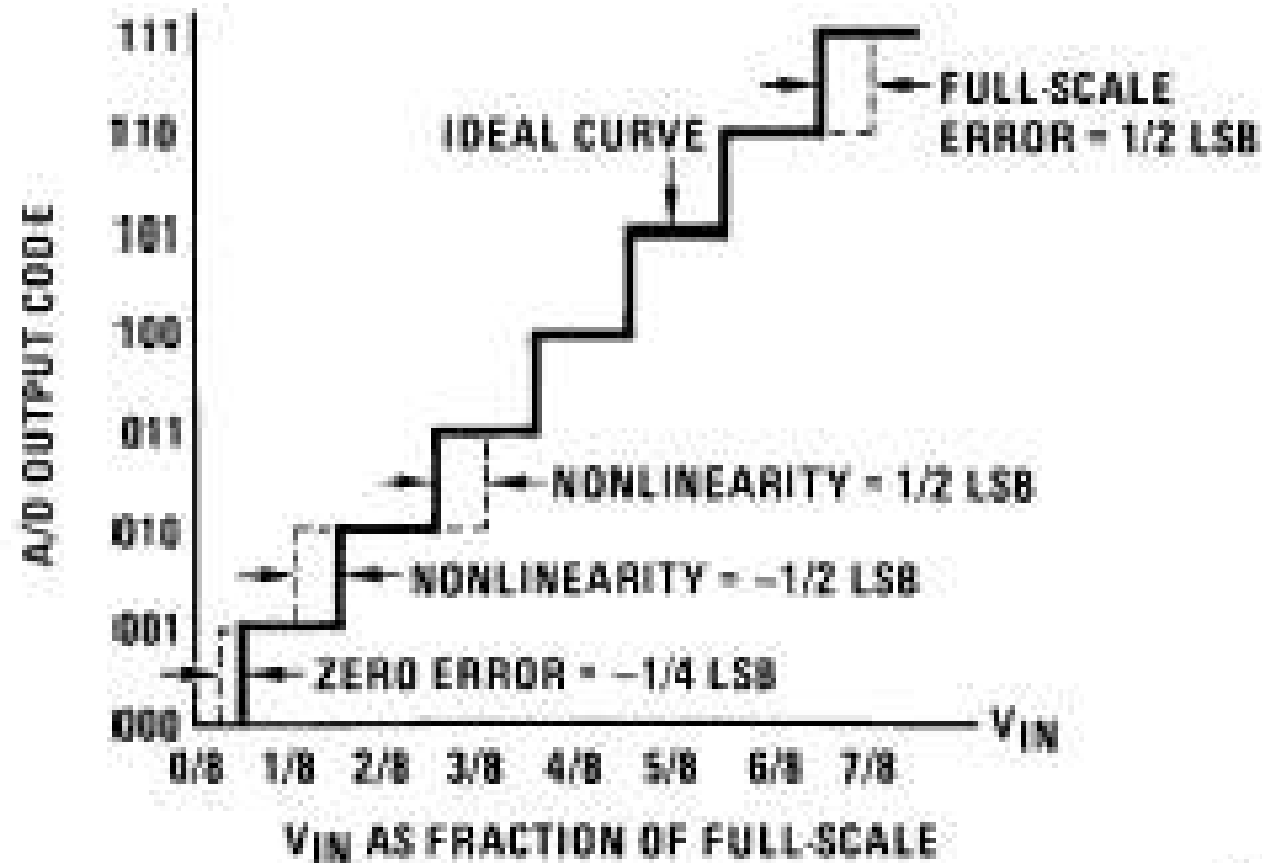

DS006672-13

FIGURE 2. 3-Bit A/D Transfer Curve

er and Switch Tree

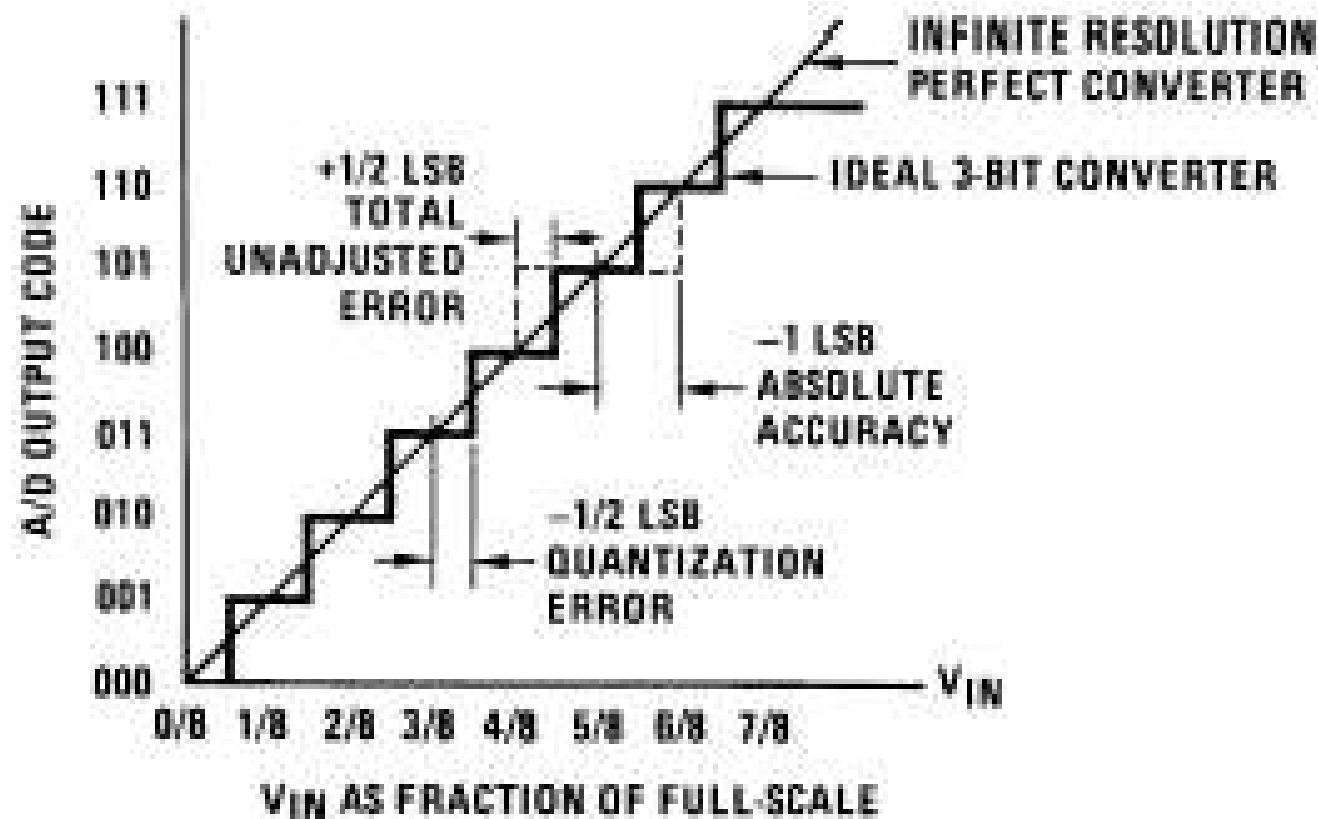

DS005672-

FIGURE 3. 3-Bit A/D Absolute Accuracy Curve