



Michigan**Engineering**



# **EECS 427**

## **Discussion 1**

---

Tuesday, September 9, 2008

# Administrative Stuff

---

- CAD1 due yesterday
- Homework 1 due Thursday, beginning of lecture
- Homework 2 due week from today – Sept. 16
  - Due at beginning of Tuesday's lecture
  - List of group members (groups typically 3-4 people)
- CAD2 due next Monday, Sept. 15
  - CAD2 again an individual assignment
  - CAD3 and on – group assignments
- Out of town again this weekend (conference)
  - Extra office hours – Friday, Sept. 12 1-3pm
  - Will be available by email again
- No discussion next Tuesday – instead, CAD3 discussed on Friday?

# Questions regarding CAD1?

??

# Layout Tips & Tricks

---

- Creating a hierarchical layout
  - Don't have to copy & paste geometries!
  - Instantiate previous layouts using **Create->Instance** (Shortcut: i)
- Viewing hierarchy
  - Two ways to change number hierarchy display on screen.
    - Through Menu
      - Options -> Display...
      - Change the Display levels
    - Through Hot Key
      - Shift+f: show all hierarchy
      - Ctrl+f: hide all hierarchy

# Layout Tips & Tricks (cont'd)

---

- Editing in hierarchy
  - Can open up layout using *Library Manager* (saved changes will be reflected after redraw – Ctrl+r)
- Can go to **Design->Hierarchy->Descend** (Shortcut: X)
  - Opens up design in current window
  - Return to previous level in hierarchy: **Design-> Hierarchy->Return** (Shortcut: B)
- Adding geometries
  - Rectangle -> r
  - Path -> p
  - Label -> l

# Layout Tips & Tricks (cont'd)

---

- Modifying geometries
  - Copy -> C
  - Move -> m (whole shape only)
  - Stretch -> s (whole shape or edge)
- Rotating and Flipping
  - After selecting copy , move, create instance, etc., HIT F3!

**\*\* Hitting F3 in any mode will pop-up the associated form\*\***

- Other useful commands

- Properties -> q
- Search -> S
- Select all -> Ctrl+a
- Deselect all -> Ctrl+d

# LSW Management

---

- By default, LSW window shows TONS of layers!!
- You can set the LSW to show only the layers that are in your layouts
  - [In Virtuoso Window] **IBM\_PDK->LSW->Present Layers Only**
- To add more layers that are not in the LSW
  - [In LSW Window] **Edit->Set Valid Layers**

# Gravity

---

- One of the functions that is turned off by default is gravity
  - **THANK GOODNESS!!**
- Gravity allows you to lock on to an edge or corner of a shape when your mouse cursor get close
  - Annoying or helpful...you be the judge!!
- To turn it on or turn it off.
  - ***Options->Layout Editor*** (Shortcut: E) in Layout view
    - Click on “Gravity On” to toggle between the on and off mode
    - Can also toggle on and off using shortcut: ‘g’

# Hierarchical Design

---

- Make sure you use hierarchical design from now on!!
  - Will make life a whole lot easier

# Circuit Design

---

- General Flow for any design
  - Schematic Creation (how is this circuit supposed to function?)
  - Symbol Generation (more specific symbols useful in hierarchy)The image shows two schematic symbols. The first is a D flip-flop symbol, which consists of a rectangle with a small circle at the top right corner and a curved arrow pointing from the bottom left to the top right. The second is a triangle symbol, which is a simple equilateral triangle with two small circles at its vertices.
- Digital Logic Simulation (does it function as expected?)
- Analog Simulation Testbench Creation (does spice backup digital simulation?)
- Layout
  - DRC
  - LVS
- PEX -> parasitic extraction
- Backannotation and Spice simulation (how does circuit behave with all of parasitics?)

# Circuit Design (cont'd)

---

- We're not done...

**ITERATE!!!!**

- Modify and possibly redesign to hit specifications (size up gates to meeting timing, relocate cells to reduce interconnect capacitance, etc.)

# Backannotation


---

- Generally in this class, backannotate to 2 places
  - Digital Simulation (Verilog)
  - Analog Simulation (Spice)
- How do we do this?
  - Already learned analog simulation (“calibre” view generation using PEX)
  - Digital simulation backannotation described in Tutorial 1.5


# Tutorial 1.5
 
## ■ Main idea

- Add Verilog delay property,  $t_d$ , to a transistor to represent some delay (e.g., CLK-Q, setup, hold)
- Use delays to get more accurate representation in simulations





## ■ Review

 

# Tutorial 1.5 (cont'd)



- How do setup and hold affect timing?

  

- $\downarrow t_{SU}$  (closer D transitions before Clk,  $\uparrow$  CLK-Q delay)

# Tutorial 1.5 (cont'd)

- How do setup and hold affect timing?

  

- $\downarrow t_{\text{hold}}$  (closer D transitions after Clk,  $\uparrow$  CLK-Q delay)

# Tutorial 1.5 (cont'd)

---

- How to measure setup and hold?
- Setup
  - Store a 1 (0) to the flip-flop and allow to settle for one clock cycle
  - Next clock cycle, change D input  $\geq 0.25$  clock cycle before rising edge and measure CLK-Q delay (50% CLK  $\rightarrow$  50% Q)
- Run parametric sweep adjusting D transition later and later
  - closer to rising edge of CLK (make sure hold time is long too,  $\geq 0.25$  clock cycle, otherwise hold will affect too!!)
- Setup constraint is time in parametric sweep which causes  $\approx 5\%$  increase in CLK-Q delay (calculated in 2<sup>nd</sup> step)

# Tutorial 1.5 (cont'd)

---

- How to measure setup and hold?
- Hold
  - Store a 1 (0) to the flip-flop and allow to settle for one clock cycle
- Next clock cycle, change D input  $\geq 0.25$  clock cycle after rising edge and measure CLK-Q (**should be similar to 2<sup>nd</sup> step of setup time**)
- Run parametric sweep make D transition earlier and earlier (making sure setup time is long,  $\geq 0.25$  clock cycle)
  - Hold constraint is time in parametric sweep which causes  $\approx 5\%$  increase in CLK-Q delay (calculated in 2<sup>nd</sup> step)

# Tutorial 1.5 (cont'd)

---


- Once we characterize setup & hold for cell, backannotate delays into Verilog simulation!!
- Further reading – Insert E (pp. 431 – 433)

**DONE!!!**

# Supplemental Slides


# Setup/Hold Time Illustrations
 
## Circuit before clock arrival (Setup-1 case)



 
# Setup/Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)



 
# Setup/Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)




 
# Setup/Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)



 
 
# Setup/Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)





# Setup/Hold Time Illustrations

## Hold-1 case

  



# Setup/Hold Time Illustrations

## Hold-1 case

  



# Setup/Hold Time Illustrations

## Hold-1 case

  

# Setup/Hold Time Illustrations

## Hold-1 case

  

# Setup/Hold Time Illustrations

## Hold-1 case

