 


EECS 427 - F08 - HW1 SOLUTIONS

1a) $NM_L = V_{IL}$ so $V_{IL} = 1.15 V$
 $NM_H = V_{DD} - V_{IH}$ $V_{IH} = 2.5 - 1.1 = 1.4 V$



V_m will fall on the sloped line, so

let's define it.

$$\text{slope} = \frac{\Delta y}{\Delta x} = \frac{-2.5}{1.4 - 1.15} = -10$$

$$V_{out} = -10 V_{in} + b$$

$$2.5 = -10 \cdot 1.15 + b \Rightarrow b = 14$$

$$\text{so } V_{out} = -10 V_{in} + 14$$

V_m occurs when $V_{out} = V_{in}$

$$V_m = -10 V_m + 14$$

$$\underline{V_m = 1.27 V}$$

By equating the NMOS + PMOS current, we get the following (see p185 of Rabaey)

$$V_m = \frac{\left(V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1+r}$$

$$\text{where } r = \frac{k'_P \left(\frac{W_P}{L} \right) V_{DSATp}}{k'_n \left(\frac{W_n}{L} \right) V_{DSATn}}$$

solve for r:
$$r = \frac{(V_m - V_{Tn} - \frac{V_{DSATn}}{2})}{(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} - V_m)} = 1.6125$$

from the defin of r, we get
$$W_n = \frac{1}{r} \cdot \frac{k'_P V_{DSATp}}{k'_n V_{DSATn}} \cdot W_P = 0.77 \mu m$$

To solve for t_{FO4} , use
$$t_{FO4} = \frac{1}{2} (t_{PLH} + t_{PHL}) = \frac{1}{2} \cdot 0.69 \cdot C_L (R_{eqP} + R_{eqn})$$

$$R_{eqn} \approx \frac{13 k\Omega}{W_n/L_{eff}} = \frac{13 k\Omega}{.77/.2} = 3.377 k\Omega \quad R_{eqP} \approx \frac{31 k\Omega}{W_P/L_{eff}} = \frac{31 k\Omega}{3/.2} = 2.067 k\Omega$$

$$C_L = \underbrace{4 C_{gc,P} + 4 C_{gc,n}}_{4 \text{ fanout inverters}} + \underbrace{\frac{1}{2} C_{gc,P} + \frac{1}{2} C_{gc,n}}_{\text{self-loading}} = 4.5 (C_{gc,P} + C_{gc,n})$$

For transistors in cutoff, $C_{gc} = C_{ox} W L_{eff}$

$$C_{gc,n} = 6 fF/\mu m^2 \cdot .77 \mu m \cdot .2 \mu m = 0.924 fF$$

$$C_{gc,P} = 6 fF/\mu m^2 \cdot 3 \mu m \cdot .2 \mu m = 3.6 fF$$

$$C_L = 4.5 (C_{gc,n} + C_{gc,P}) = 4.5 (.924 + 3.6) = 20.358 fF$$

$$t_{FO4} = \frac{1}{2} \cdot .69 C_L (R_{eqP} + R_{eqn}) = \frac{1}{2} \cdot .69 \cdot 20.358 \cdot 10^{-15} (3.377 + 2.067) \cdot 10^3 = \boxed{38.2 ps}$$

1b) Since $\frac{W_p}{W_n} = 2.5$ and we want equivalent rise and fall transitions for this problem, we need $\frac{W_p}{W_n} \approx 2.5 \therefore W_p = 2.5 W_n$

- Delay through first inverter:

$$t_p = \frac{1}{2} \cdot 69 C_L (R_{eqn} + R_{eqp}) = .345 \left(\frac{13000}{1/.2} + \frac{31000}{2.5/.2} \right) C_L = 1752.6 C_L$$

$$\begin{aligned} C_L &= \frac{1}{2} [C_{gs,p,inv1} + C_{gs,n,inv1}] + C_{L,1} + C_{gs,p,inv2} + C_{gs,n,inv2} \\ &= \frac{1}{2} [C_{ox} W_{p,inv1} L_{eff} + C_{ox} W_{n,inv1} L_{eff}] + C_{L,1} + C_{ox} W_{p,inv2} L_{eff} + C_{ox} W_{n,inv2} L_{eff} \\ &= \frac{1}{2} \cdot 6 \text{ fF}/\mu\text{m}^2 \cdot .2 \mu\text{m} (2.5 \mu\text{m} + 1 \mu\text{m}) + 10 \text{ fF} + 6 \text{ fF}/\mu\text{m}^2 \cdot .2 \mu\text{m} (W_{p,inv2} + W_{n,inv2}) \\ &= 12.1 + 1.2 (W_{p,inv2} + W_{n,inv2}) \quad \text{with } W_p = 2.5 W_n \quad C_L = 12.1 + 4.2 W_{n,inv2} \quad \text{in fempto} \end{aligned}$$

$$\text{so } t_{p,inv1} = 1752.6 (12.1 + 4.2 W_{n,inv2}) \times 10^{-15}$$

- Delay through second inverter:

$$t_{p,inv2} = \frac{1}{2} \cdot 69 \cdot C_L (R_{eqn} + R_{eqp}) = .345 \left(\frac{13000}{W_n/.2} + \frac{31000}{2.5 W_n/.2} \right) C_L = \frac{1752.6}{W_n} \cdot C_L$$

$$C_L = 40 \text{ fF} + \frac{1}{2} [6 \text{ fF}/\mu\text{m}^2 \cdot .2 \mu\text{m} \cdot 3.5 W_n] = 40 + 2.1 W_n$$

$$t_{p,inv2} = \frac{1752.6}{W_n} (40 + 2.1 W_n) \times 10^{-15}$$

$$t_p = t_{p,inv1} + t_{p,inv2}$$

This is minimized when $W_n \approx 3.09 \mu\text{m}$ $W_p = 2.5 W_n = 7.73 \mu\text{m}$

2) a) In the worst case, Flop1 $\rightarrow$ Flop2 will see negative skew.

$$\text{Flop1} \rightarrow \text{Flop2}: T = T_{\text{CLK-Q}} + T_{\text{LOGIC1}} + T_{\text{SETUP}} - (-\delta) = 150 \text{ ps} + 1500 \text{ ps} + 75 \text{ ps} + 75 \text{ ps} = 1800$$

$$\text{Flop2} \rightarrow \text{Flop3}: T = 150 + 80 + 75 + 75 = 380 \text{ ps}$$

Flop1 $\rightarrow$ Flop2 is the worse path, and sets the max frequency.

$$f = \frac{1}{T} = \frac{1}{1800 \text{ ps}} = \boxed{556 \text{ MHz}}$$

b) Since the Flop2 $\rightarrow$ Flop3 path has lower delay, it is limiting.

$$T_{\text{hold}} < T_{\text{CLK-Q}} + T_{\text{LOGIC2}} + \delta$$

$\searrow$ In worst case, δ is positive!

$$T_{\text{hold}} < 150 \text{ ps} + 80 \text{ ps} + 75 \text{ ps}$$

$$\boxed{T_{\text{hold, max}} = 305 \text{ ps}}$$

3) Ignoring skew/jitter,

$$T = T_{CLK-Q} + T_{LOGIC} + T_{SETUP} = 200 + \frac{1600}{t} + 1000 + t$$

T_{min} occurs when $t = 40$ ps

$$T_{min} = 200 + \frac{1600}{40} + 1000 + 40 = 1280 \text{ ps}$$

$$f_{max} = \frac{1}{T_{min}} = \boxed{781.25 \text{ MHz}}$$

4) a) $X = (A+B+C)(D+E)F + GH$ Rewrite in a more "CMOS-friendly" form


$$= \overline{(A+B+C)(D+E)F + GH}$$

$$= \overline{(A+B+C)(D+E)F \cdot GH}$$

$$= \overline{[A+B+C + D+E + F][G+H]}$$

$$= (\overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{D} \cdot \overline{E} + \overline{F})(\overline{G} + \overline{H})$$

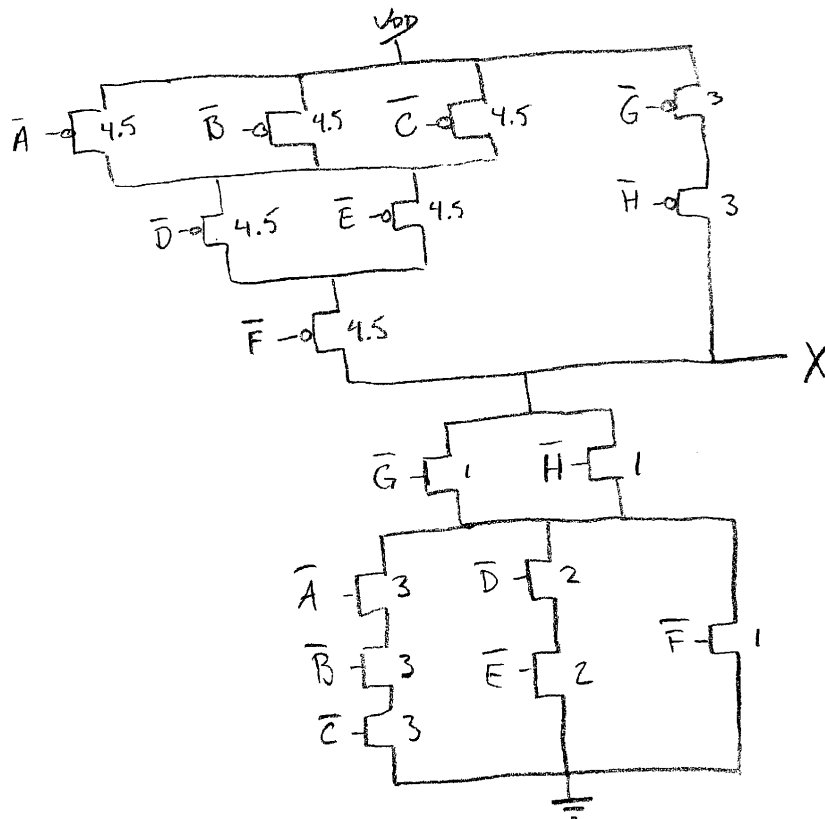Size all paths to be $W_P/W_N = \frac{1.5}{.5}$



Numbers are transistor widths, in microns.

b)

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

XNOR $Y = A \oplus B$

5) Lets say that all power is consumed when a node goes high (actually, $\frac{1}{2}$ is consumed when it goes high, $\frac{1}{2}$ when it goes low, but you will get the same answer both ways)

so $P_{\text{dyn}} = C_L V_{DD}^2 f_{0 \rightarrow 1}$ where $f_{0 \rightarrow 1}$ is the frequency of $0 \rightarrow 1$ transitions
 $[f_{0 \rightarrow 1} = f \alpha_{0 \rightarrow 1}]$

Let's first find the percentage of cycles when node n_3 goes high. This will happen if previously $\{n_0, n_1\} = \{0, 0\}$ and one or both inputs go high.

Probability $(\{n_0, n_1\} = \{0, 0\}) = 0.25$

$P(n_0 \text{ stays } 0, n_1 \text{ goes } 0 \rightarrow 1) = 0.9 \times .1 = .09$

$P(n_0 \text{ goes } 0 \rightarrow 1, n_1 \text{ stays } 0) = .1 \times .9 = .09$

$P(n_0 \text{ goes } 0 \rightarrow 1, n_1 \text{ goes } 0 \rightarrow 1) = .1 \times .1 = .01$

So probability $(\{n_0, n_1\} = \{0, 0\})$ AND the output n_3 goes high is
 $0.25(.09 + .09 + .01) = \underline{0.0475}$

Now, let's do the same for n_4 . n_4 can go high if

a) inputs are $(0, 0)$ and they both go high $(0 \rightarrow 1, 0 \rightarrow 1)$

b) inputs are $(0, 1)$ and n_3 goes high $(0 \rightarrow 1, 1 \rightarrow 1)$

c) inputs are $(1, 0)$ and n_2 goes high $(1 \rightarrow 1, 0 \rightarrow 1)$

a) $P(n_3 = 0, n_2 = 0) = \frac{1}{8}$ $P(0 \rightarrow 1, 0 \rightarrow 1) = .0475 \times .1 = .00475$

so probability of (a) is $\frac{1}{8} \cdot .00475 = .00594$

b) $P(n_3 = 0, n_2 = 1) = \frac{1}{8}$ $P(0 \rightarrow 1, 1 \rightarrow 1) = .0475 \times .9 = .04275$

Probability of (b) is $\frac{1}{8} \cdot .04275 = .00534$

c) $P(n_3 = 1, n_2 = 0) = \frac{3}{8}$

but what's the probability that n_3 stays a 1?

$P(n_3 \text{ is a } 1 \text{ and stays a } 1) = 1 - P(n_3 \text{ is a } 1 \text{ and transitions})$

$P(n_3 \text{ is a 1 and transitions to } \emptyset)$:

$$P(n_0=0, n_1=1) = 1/4 \quad P(0 \rightarrow 0, 1 \rightarrow 0) = .9 \times .1 = .09$$

$$P(n_0=1, n_1=0) = 1/4 \quad P(1 \rightarrow 0, 0 \rightarrow 0) = .1 \times .9 = .09$$

$$P(n_0=1, n_1=1) = 1/4 \quad P(1 \rightarrow 0, 1 \rightarrow 0) = .1 \times .1 = .01$$

Since $P(n_0=0, n_1=1) = P(n_0=1, n_1=0) = P(n_0=1, n_1=1)$

given that $n_3=1$, the probability n_3 transitions is $\frac{.09 + .09 + .01}{3} = .06\bar{3}$

using this to find out (c) above,

$$c) \quad P(n_3=1, n_2=0) = 3/8 \quad P(1 \rightarrow 1, 0 \rightarrow 1) = .06\bar{3} \times .1 = .006\bar{3}$$

So the probability n_4 goes $0 \rightarrow 1$ is (from (a), (b), and (c))

$$.00594 + .00534 + .00633 = 0.0176$$

Now, assuming that power is only used in this circuit when n_3 and n_4 switch,

$$P_{\text{dyn}} = C_L V_{DD}^2 f \alpha_{0 \rightarrow 1} = 10\text{fF} \times (2.5\text{V})^2 \cdot 16\text{Hz} \cdot (.0475 + .0176) \\ = \boxed{4.1 \mu\text{W}}$$

If you want to include n_0 , n_1 , and n_2 , you will get

$$P_{\text{dyn}} = 10\text{fF} (2.5\text{V})^2 \cdot 16\text{Hz} \cdot (.0475 + .0176 + .05 + .05 + .05)$$

↑ remember we're only looked at $0 \rightarrow 1$ transitions

$$= \boxed{13.4 \mu\text{W}}$$