
EECS 427

Lecture 10: Power/Energy in CMOS Reading: 5.5, 6.3

Outline

- Last time:
 - Adders: Carry select, square-root, log-adders
- Today:
 - Power Dissipation in CMOS
- Sample Logical Effort Questions posted


Overview

- Power and energy in CMOS
 - Why is power/energy reduction important
 - What constitutes total power dissipation
 - Arriving at the equations for dissipation
 - Popular approaches to power reduction
- Dynamic logic
 - Alternative to static CMOS
 - Used in industry for very high-speed circuits

Why is Power Reduction Important

- Maintaining chip temperature requires more expensive
 - Packaging: Ceramic vs Plastic for example
 - Heat Sinks
- Power Costs
 - Kilowatt hour costs are increasingly important due to improving performance/server and fairly stable performance/watt.
 - Electricity cost can easily be 40% of total cost. Current trends indicate a further increase in this percentage.
- Power delivery
 - Itanium consumes 130W at 1.3V
 - IR and $L di/dt$ drops reduce supply at devices
- Battery Life
 - Low **energy** extremely critical for mobile/hand-held applications
 - Li-ion batteries: 100-150Whr/kg. Size/Battery life trade-off.
- Niche applications
 - Many automotive circuits are hermetically sealed. Severe constraints on heat exchange result in desire of inherently lower power circuits.


Power Density in VLSI

 

Where Does the Power Go?

- Dynamic Power
 - Switching Power
 - Charging and discharging of capacitors
 - Short-circuit Power (Crowbar)
 - During switching transients, current flows between V_{dd} and GND
 - Not dominant – typically assumed to be ~10% of dynamic power
- Static Power
 - Power consumed when there is no switching
 - Leakage: due to non-ideal switches
 - Gradually becoming the dominant component
 - Important during standby

 A look at energy dissipation: RC series circuit



- Energy stored equals energy dissipated *in this case*.
- But charge is delivered by non-linear devices in CMOS circuits.
- How does that change the result?
- Is there a device independent way of figuring out the dissipation??

$$E_C = \frac{1}{2} C V_0^2$$

$$E_{diss}(R) = \int_0^{\infty} V_R \bullet I \, dt$$

$$E_{diss}(R) = \int_0^{\infty} I^2 R \, dt$$


$$E_{diss}(R) = \int_0^{\infty} \frac{V_0^2}{R^2} e^{\frac{-2t}{\tau}} R \, dt$$

$$E_{diss}(R) = \frac{V_0^2}{R} \bullet \frac{\tau}{2} \left[-e^{\frac{-2t}{\tau}} \right]_0^{\infty}$$

$$E_{diss}(R) = \frac{1}{2} C V_0^2 = E_C$$

Switching Power

- Output 0-1 transition

 


Energy drawn from supply =

Energy stored in C_L =

Energy dissipated in pulldown device =

Switching Power

- Output 0-1 transition

 



Energy drawn from supply =

Energy stored in C_L =


Energy dissipated in pulldown device =

Switching Power

  - Over an entire charge-discharge sequence then ...
 - Energy drawn from the supply =
 - Energy dissipated in the inverter =
- Energy provided by the supply is a straightforward way of tracking energy dissipation.
- But what if all load capacitance is not coupled to ground?





Switching Power

 

	Energy (supply)	Energy (PMOS)	Energy (NMOS)
Input 1→0			
Input 0→1			
Total			

Short Circuit Power (Crowbar)


- Rise and fall times are not ideal
 - Both nMOS and pMOS conducting between V_{tn} and $(V_{dd} - |V_{tp}|)$

  

Energy dissipated =


Short circuit power =

Static Power Consumption

 

Wasted energy ...
Should be avoided as much as possible
 
$$I_{sub} \approx k_0 \frac{W}{L} e^{\frac{V_{gs}' - \zeta V_{ds} - \gamma W_{sb}}{V_T}} \left(1 - e^{-\frac{V_{ds}}{V_T}} \right)$$



Total power dissipation

$$P \approx V_{dd} \bullet k_0 \frac{W}{L} e^{\frac{nV_{gs}' - \zeta V_{ds} - \gamma V_{sb} - V_{th}}{V_T}} \left(1 - e^{\frac{V_{ds}}{V_T}} \right) + s C V_{dd}^2 f + V_{dd} I_{sc} t_{sc} f$$

- Total power dissipation is the combination of all three main sources of power dissipation.
 - Dynamic switching power
 - Dynamic short-circuit current (crowbar)
 - Static leakage (sub-threshold, junction)

Common methods for power minimization

$$P \approx V_{dd} \bullet k_0 \frac{W}{L} e^{\frac{nV_{gs}' - \zeta V_{ds} - \gamma V_{sb} - V_{th}}{V_T}} \left(1 - e^{\frac{V_{ds}}{V_T}} \right) + s C V_{dd}^2 f + s V_{dd} I_{sc} t_{sc} f$$

← Static Dissipation
← Dynamic Dissipation

- Power minimization
 - Switching power usually dominates dynamic dissipation (Crowbar power accounts for about 10-15% of total dynamic dissipation)
 - Static leakage can dominate systems with low switching activity.
 - Typical value of s in datapaths is 10-20%
 - Important in systems with significant stand-by time

Common methods for power minimization

$$P \approx k_0 V_{dd} \frac{W}{L} e^{\frac{nV_{gs}' - \zeta V_{ds} - \gamma V_{sb} - V_{th}}{V_T}} + s C V_{dd}^2 f$$

$\longleftrightarrow$ Leakage Power Dissipation $\longleftrightarrow$ Switching power

- Power minimization techniques usually involve controlling one of s , C , V_{dd} , f , V_{th} as per equation
- Such changes often involve tradeoffs (eg. area, power, complexity)

Leakage Power Dissipation Switching power


- Extremely important term in switching power.
- Clock gating ($s = 2$ for clock nets)
- Gate sizing: Size down gates in non-critical paths (delay “wall”)
- Glitch avoidance
- Bus encoding / Data encoding
- Avoiding pre-charging/dynamic mechanisms or use conditional discharge (eg. in flip-flops)

Altering V_{dd} for low power dissipation

$$P \approx k_0 \underbrace{V_{dd} \frac{W}{L} e^{\frac{nV_{gs} + \zeta V_{ds} - V_{sb} - V_{th}}{V_T}}}_{\text{Leakage Power Dissipation}} + \underbrace{sC V_{dd}^2 f}_{\text{Switching power}}$$

- Supply Voltage provides quadratic reduction in switching **energy**.
- Voltage scaling results in increased delay.
- Voltage-scaling (through sizing or pipelining)
- Dynamic voltage-scaling (at runtime)
- Low-swing logic/signaling (harms noise margins)
- CVS (Clustered Voltage Scaling)

Lower V_{dd} Increases Delay

 

$$T_d = \frac{C_L * V_{dd}}{I}$$

$$I \sim (V_{dd} - V_t)^2$$

$$\frac{T_d(V_{dd}=2)}{T_d(V_{dd}=5)} = \frac{(2) * (5 - 0.7)^2}{(5) * (2 - 0.7)^2} \approx 4$$

The exponent will change next time we see this...

- Relatively independent of logic function and style.

Altering f for low power dissipation


$$P \approx k_0 V_{dd} \frac{W}{L} e^{\frac{nV_{gs}' - \zeta V_{ds} - \gamma V_{sb} - V_{th}}{V_T}} + s C V_{dd}^2 f$$

←—————→
←—————→

Leakage Power Dissipation Switching power


- Scaling the frequency reduces switching power
- Switching **energy** remains unchanged.
- However, leakage energy dissipation is increased
- Scaling only frequency does not achieve energy reduction
 - For the same application, energy dissipation actually increases
- A possible option for high performance cores which cannot transfer heat away from the chip fast enough.

Reducing V_{th} to offset delay penalty

 

Leakage as a Function of V_T

 - Reducing the V_T **increases** the sub-threshold leakage current (exponentially)
 - ~90mV reduction in V_T increases leakage by 10X
- But, reducing V_T **decreases** gate delay (increases performance)



Altering V_{th} for low power dissipation

$$P \approx k_0 V_{dd} \frac{W}{L} e^{\frac{nV_{gs}' - \zeta V_{ds} - \gamma V_{sb} - V_{th}}{V_T}} + s C V_{dd}^2 f$$

$\xleftarrow{\hspace{10em}}$ Leakage Power Dissipation $\xrightarrow{\hspace{10em}}$ Switching power

- Dual V_{th} design
 - Determine the critical paths during the design phase, use low V_T devices on those paths for speed (requires dual-Vt, variation issues)
 - Use a high V_T in rest of logic to control leakage
 - Can provide total leakage reduction of up to 80%
- Body biasing
 - Change the substrate potential to reduce leakage current
- MTCMOS
 - Use the “stack effect” and high V_{th} devices to achieve leakage reduction
 - Performance degradation (frequency, start-up time)

Summary

- Power reduction is as important as increasing speed in IC design today.
- Three major components of power in CMOS
 - Dynamic: charging capacitors → dominant
 - Short-circuit: small, typically ignore
 - Static: subthreshold leakage, growing fast already dominant in certain structures (eg. memories)