
EECS 427

Lecture 6: Logic Effort

Back of the envelope gate sizing
Reading : Sutherland et. Al “Logical Effort”

Outline: logic effort

- Motivation and intuition
- Model the delay of one gate
- The delay of a chain of gates (multistage)
- Branching
- Minimum delay
- Best number of stages and gate sizing
- Complex gates
- Asymmetric gates
- Unequal rise and fall times
- Examples
- Limitations

Logical Effort motivation

- Sizing of a chain of inverters
 - Geometric progression
- How about more complex logic?
- Logical Effort objectives:
 - Quick & dirty, back of the envelope sizing
 - Make trade-off between circuits
- Reference:
 - I. Sutherland, B. Sproull, D. Harris, *Logic Effort - designing fast CMOS Circuits* Academic Press, 1999



Delay : Output / Input load

Let's model the delay as a function of the output / input load

$$D \approx RC_{sl} + RC_{in} \frac{C_{out}}{C_{in}}$$

Define

$$h = \frac{C_{out}}{C_{in}}$$

 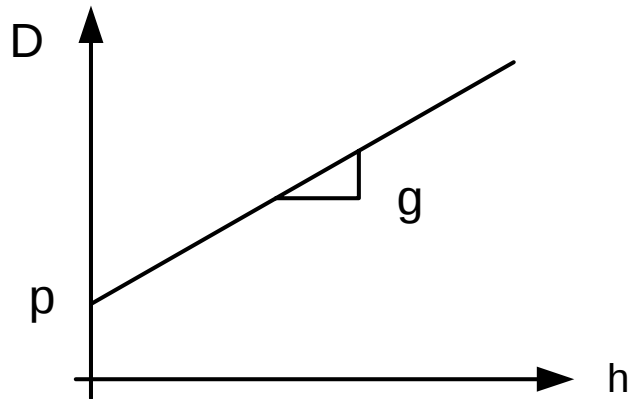

$$D \approx \underbrace{RC_{sl}}_p + \underbrace{RC_{in}}_g \cdot h$$

$$D \approx p + g \cdot h \qquad f = g \cdot h$$

p = Parasitic (intrinsic) delay

g = Logical effort

h = Electrical effort

f = Effort delay or Stage effort

Figure of Merit

- Assume that rise delay = fall delay
 - Simplifying assumption, of reducing relevance
 - Therefore $R_p(\text{inv}) = R_n(\text{inv})$
- Consider the RC product of a minimum sized gate.
 - $R_0 = R_p = R_n$
 - $C_0 = C_{in}$ (total input capacitance)
- As W varies as $kW_{\min}$,
 - RC product = $1/kR_0 * kC_0 = R_0C_0$

Figure of Merit - Inverter

- Consider an inverter with equal rise and fall delay.
 - Remember that size does not matter for figure of merit
 - For the sake of simplicity, consider a minimum sized inverter, $W_p = 2W_n = W_{\min}$
 - $C_{\text{in}} = C_n + C_p = C_{\min} + 2C_{\min} = 3C_{\min}$
 - $R_{\text{eff}} = R_{\min}$
 - $\tau = R_{\min} C_{\min}$
 - RC product (in units of τ) = 3
- Evaluate all RC products in the same units to get delay
- In addition, by using a figure of merit which is relative to the inverter RC product, we get delay in units of inverter delay.

Units of effort

- Reference is the inverter:

$$g_{inv} = 1$$


$$p_{inv} = 0.6$$

- g is a function of the complexity of a gate, not its size
 - Additional delay from driving its own input loading
- p is a function of the technology
 - Unloaded delay of a gate


Logical effort

- Logic effort can be thought of the size of a gate relative to an inverter to produce the same output current as an inverter with the same output load

1. Inverter

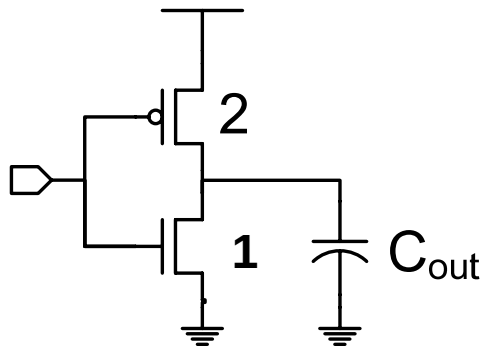

2. 2-input NAND

 

$$f_1 = f_2$$

$$g_1 h_1 = g_2 h_2$$

$$1 \frac{C_{out}}{3C} = g_2 \frac{C_{out}}{4C}$$

$$g_2 = \frac{4}{3}$$

$$C_{sd,inv} = 3C$$

$$C_{sd,nand} = 6C$$

$$p_2 = 2p_{inv}$$


Logical effort (g)

Gate type	Number of inputs					
	1	2	3	4	5	n
Inverter	1					
NAND		$4/3$	$5/3$	$6/3$	$7/3$	$(n + 2)/3$
NOR		$5/3$	$7/3$	$9/3$	$11/3$	$(2n + 1)/3$
Multiplexer		2	2	2	2	2
XOR (parity)		4	12	32		


Parasitic Delay (p)

Gate type	Parasitic Delay
Inverter	p_{inv}
n-input NAND	$n \cdot p_{\text{inv}}$
n-input NOR	$n \cdot p_{\text{inv}}$
n-way multiplexer	$2n \cdot p_{\text{inv}}$
XOR, XNOR	$4 \cdot p_{\text{inv}}$

Delay components

 

F04 Example

 

$$C_{out} = 4C_{in}$$


$$h = 4$$

$$g = 1$$

$$p = 0.6$$

$$D = 4 + 0.6 = 4.6\tau$$

More complex circuit

 


$$h = 3$$

$$g = \frac{6}{3}$$

$$p = 4 \times 0.6$$

$$D = 8.4\tau$$

Multistage effort

 

Defining the path effort H as:

$$H = \frac{C_3}{C_1}$$

$$h_1 = \frac{C_2}{C_1}$$

$$h_2 = \frac{C_3}{C_2}$$



$$H = h_1 h_2$$

What was that homework problem all about??

- Recap of Question : Minimize the perimeter of a rectangle with dimensions w, h , for a constant area.
- Result is clearly a square.
- Corollary of a specific optimization problem which minimizes the sum of variables given the constraint that the product is constant


Minimum delay

Total delay

$$D = g_1 h_1 + p_1 + g_2 h_2 + p_2$$

Substitute H
 
$$D = g_1 h_1 + p_1 + g_2 \frac{H}{h_1} + p_2$$



$$\min\{D\} \Rightarrow \frac{\partial D}{\partial h_1} = g_1 - g_2 \frac{H}{h_1^2} = 0$$

Minimize the delay

$$g_1 - g_2 \frac{h_2}{h_1} = 0$$


Solve for the minimum delay

$$g_1 h_1 = g_2 h_2$$

$$f_1 = f_2$$

Delay is optimal when the stage efforts are equal

Branching

 

Without branching: $H = h_1 h_2$

With branching: $h_2 = \frac{C_3}{C_2}$

$$h_1 = \frac{3C_2}{C_1}$$

$$h_1 h_2 = 3H$$

$$b_i = \frac{C_{on-path} + C_{off-path}}{C_{on-path}} \quad \rightarrow$$

$$C_{on-path,2} = C_2$$

$$C_{off-path,2} = 2C_2$$

$$b_2 = \frac{3C_2}{C_2} = 3$$

Equivalent Path Efforts

$$H = \frac{C_{out}}{C_{in}}$$

Path Effort

$$B = \prod b_i$$

$$\prod h_i = BH$$

$$G = \prod g_i$$

$$F = GBH = \prod g_i h_i$$

Path Effort:

- Does not change with added inverters
- Does not depend on sizes, but on topology

Minimum Delay

$$F = GBH = \prod g_i h_i$$

Stage effort of stage i: f_i

$$g_i h_i = f_i$$

Optimal stage effort is:

$$\hat{f} = f_i$$

For N stages:


$$F = \hat{f}^N \Rightarrow \hat{f} = F^{1/N}$$

Minimum Delay:

$$\hat{D} = \sum_i g_i h_i + p_i$$

$$\hat{D} = N\hat{f} + \sum_i p_i = N\hat{f} + P$$

Example: compute min. delay

 

$$G = g_a g_b g_c = \left(\frac{4}{3}\right)^3 = 2.37$$

$$B = 1$$

$$H = C_L / C_{in} = 1$$

$$F = GBH = 2.37$$

$$\hat{f} = F^{1/3} = 4/3$$

$$\hat{D} = 3(2.37)^{1/3} + 3(2p_{inv})$$

$$\hat{D} = 4 + 6 \times 0.6 = 7.6\tau$$

Summary

- Instruction set and general 2-stage pipeline structure of the baseline processor
 - More on this in upcoming discussions
- Logic Effort:
 - Delay of an individual gate
 - Path delay
 - Minimum path delay