

# Low Area Dual-band LNA with Active Inductor for GSM applications

---


Hyungil Chae, Justin Shaler

EECS 522 W09


# Motivation & Application

- Different cell phone bands are used over countries
  - GSM-850: 880MHz, 25MHz bandwidth
  - GSM-1900: 1.96GHz, 60MHz bandwidth
  - Dual band LNA for device compatibility
- Inductors consume large area on analog chip
  - Bad for yield on wafer, increases unit cost
  - Try to reduce number of inductors

# Design Overview

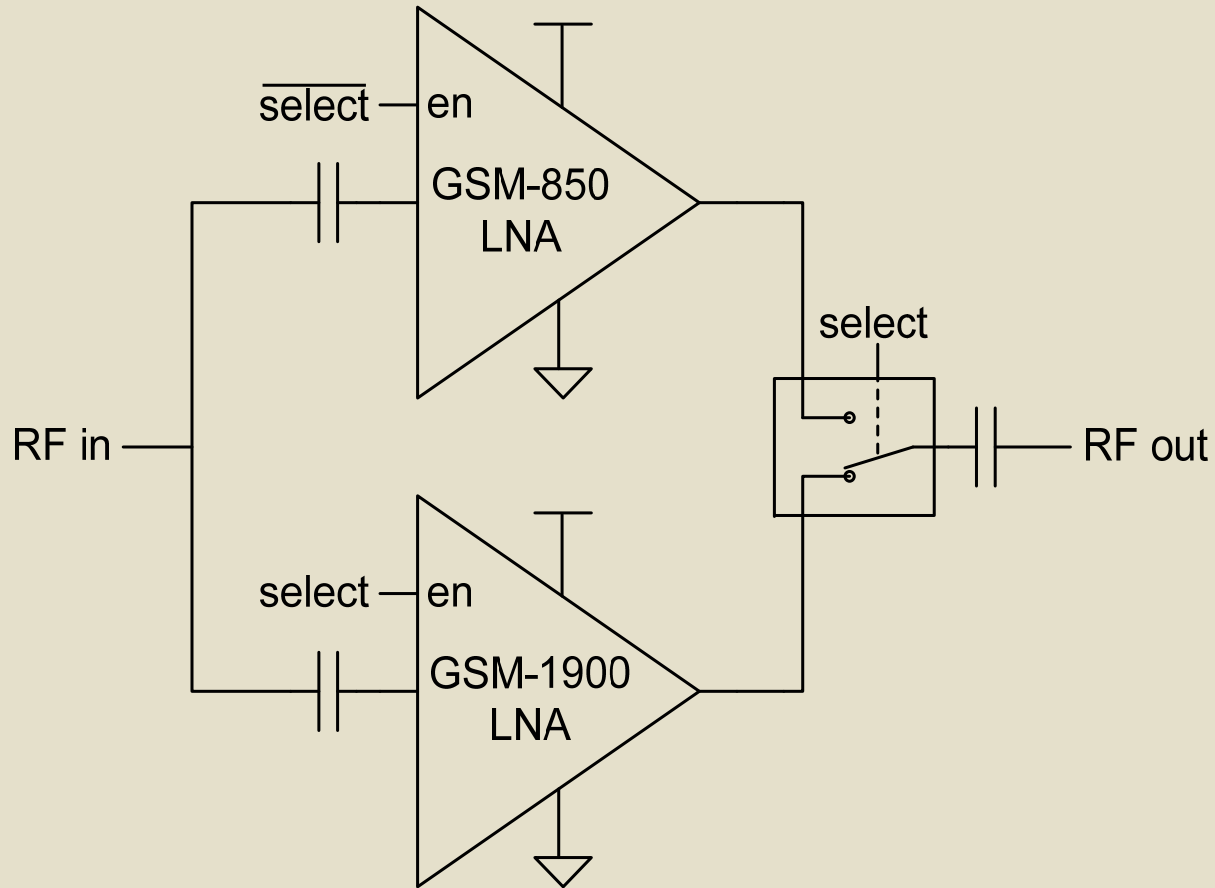


# 1.96GHz-Band Schematic

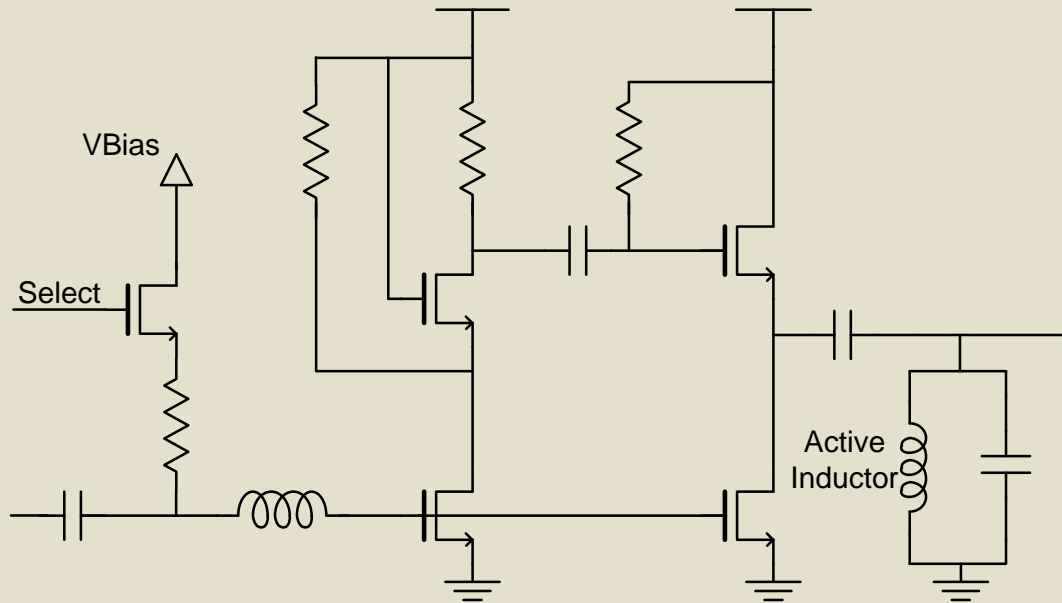


- Two stage for isolation
- Active inductor at load
- $Select = 1$

# Band Selection

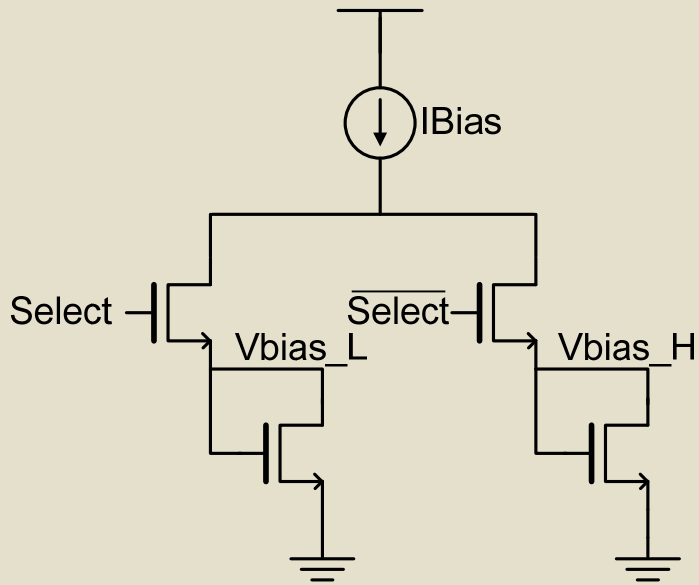

Bias voltage control at  
LNA input

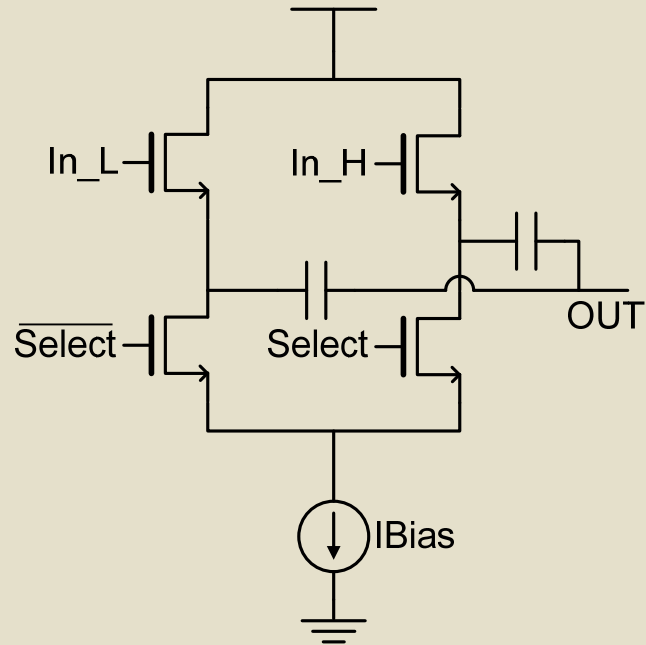

Output gating for  
isolation


# Inductor Options

Type	Inductance	Area	Quality Factor	Repeatability	Noise
None	0	Small	N/A	Good	Good
On-chip spiral	0.2 to 50nH	Large	20	Good	Fair
External discrete	1 to 150nH	Large	150	Fair	Fair
Bond-wire	0.5 to 5nH	Small	150	Poor	Fair
On-chip active	1 to 200nH	Small	0-600, tunable	Good	Poor

(Values for  $f < 2\text{GHz}$ )


# Active Inductor Design

Active Inductor

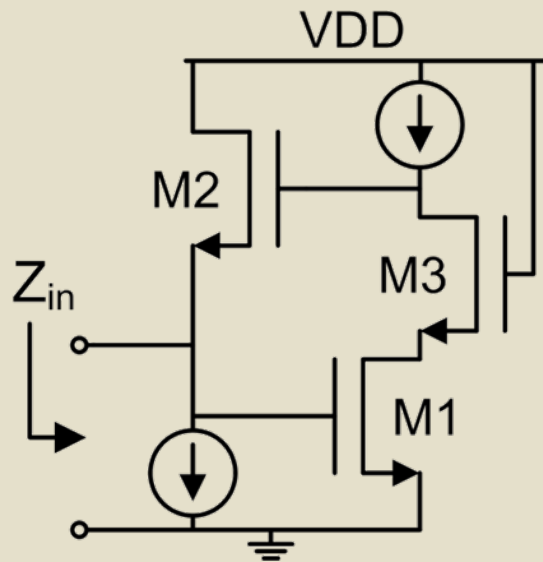

$$Z_{in} = \frac{1}{sC_{gs1}} \parallel \frac{1 + sC_{gs2}r_{o1}}{(1 + g_{m1}r_{o1})(g_{m2} + sC_{gs2})}$$


Equivalent Circuit

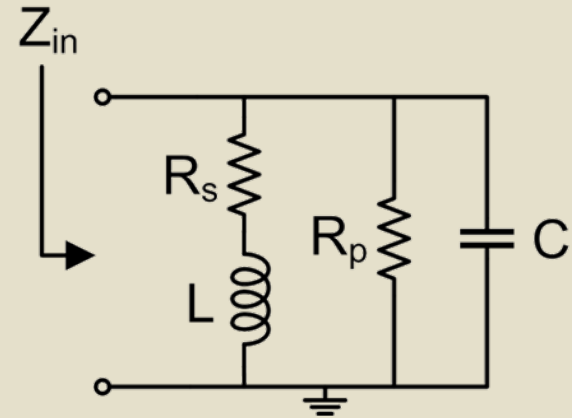

$$L = \frac{C_{gs2}}{g_{m1}g_{m2}}$$

$$R_s = \frac{1}{g_{m1}g_{m2}r_{o1}r_{o2}g_{m3}}$$

# Active Inductor Results

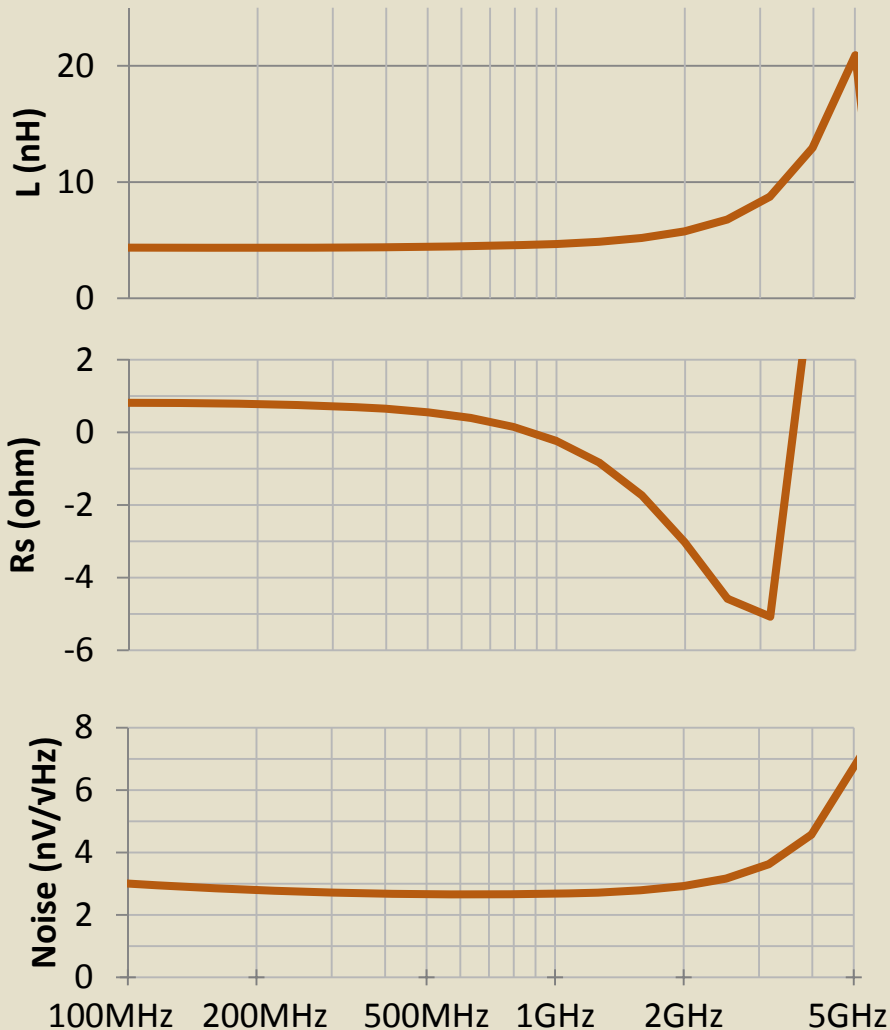

$L = 4.59\text{nH}$  at 880MHz

$R_s = -24.06\text{m}\Omega$


Compensate by adding  
external series resistance

Noise voltage =  $2.67\text{nV}/\sqrt{\text{Hz}}$


Tolerable when active  
inductor is at LNA output




# Input Matching ( $S_{11}$ )

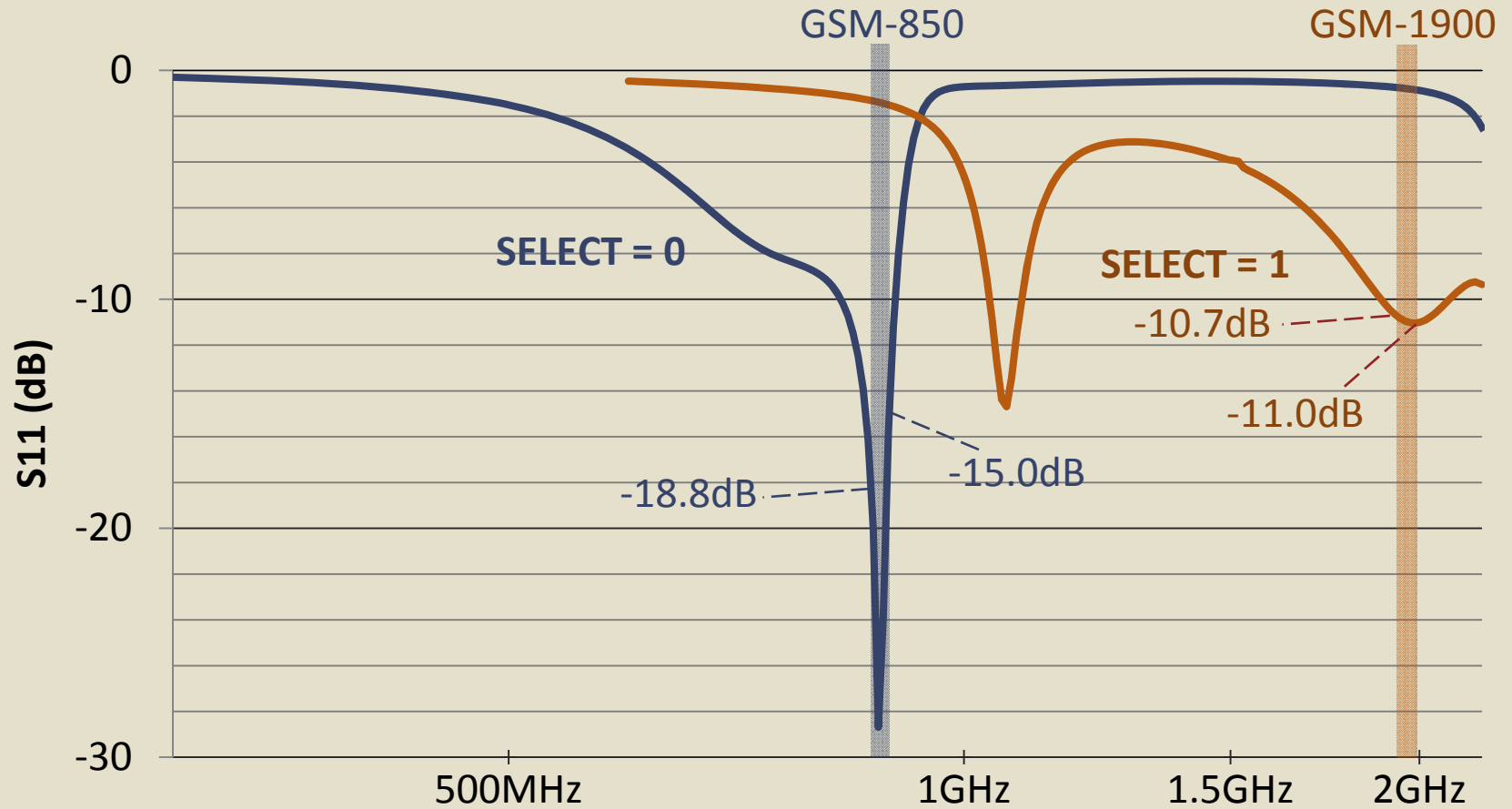

# Gain ( $S_{21}$ )

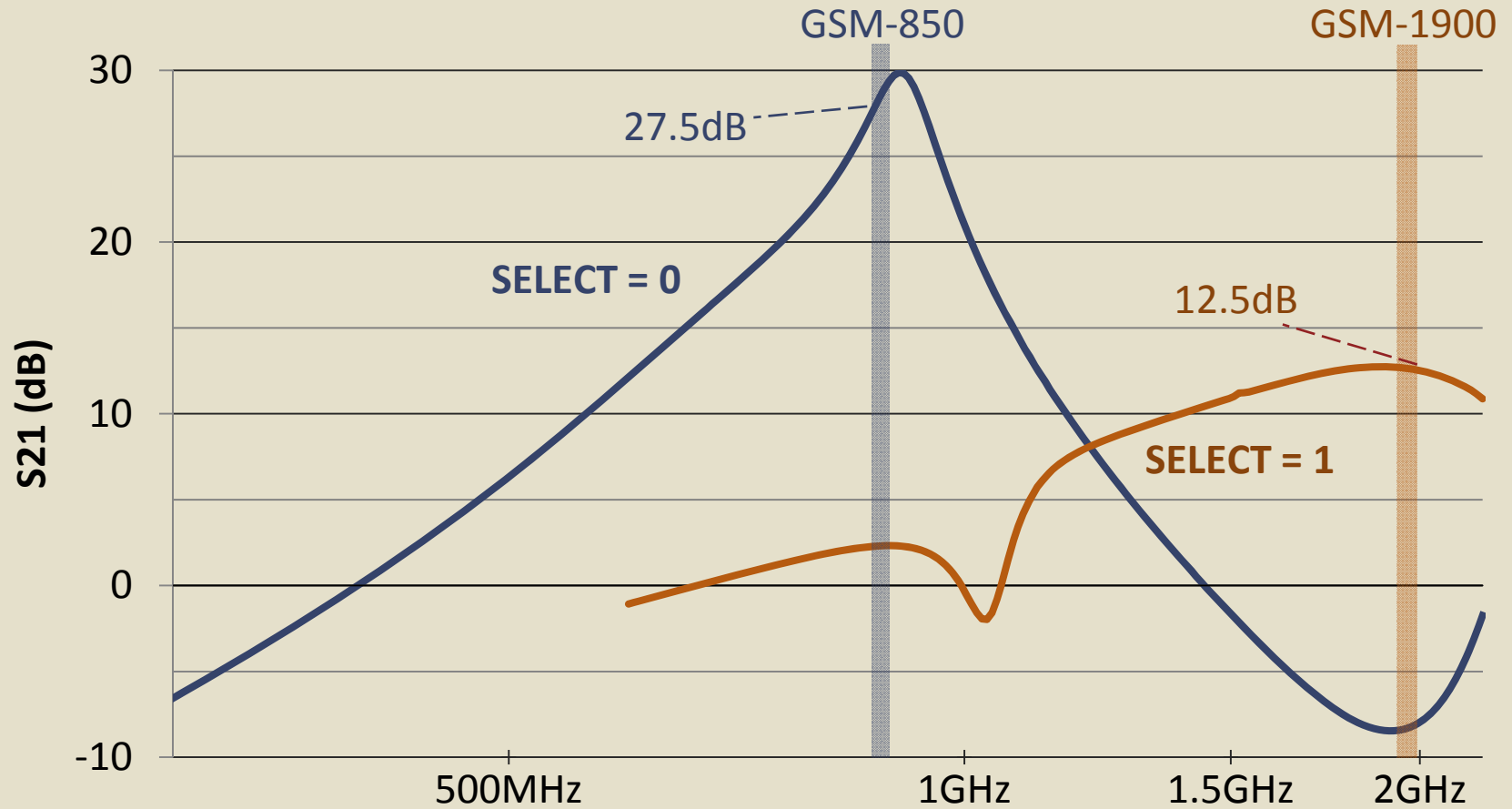


# Noise Figure

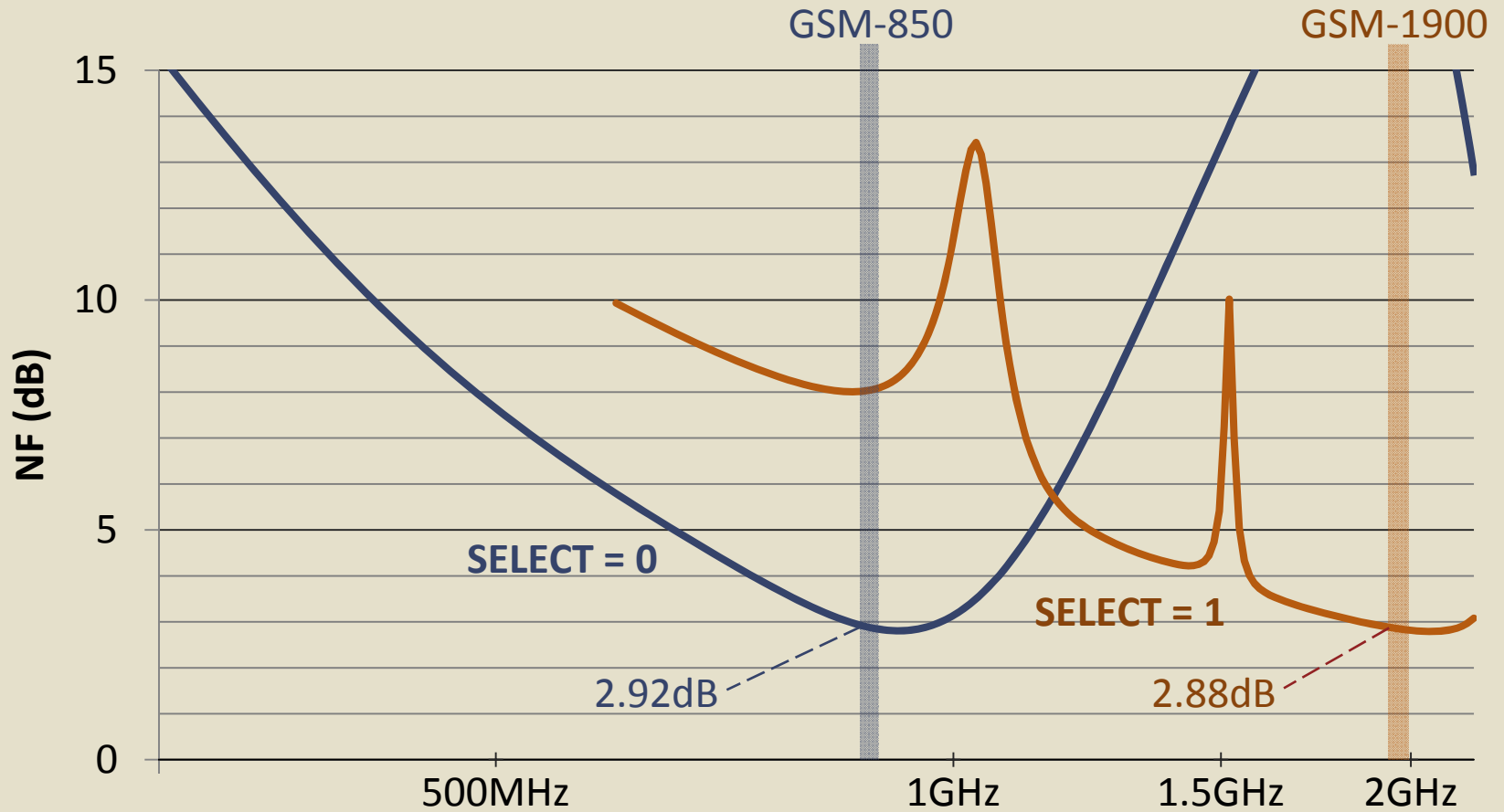

# Layout

720um

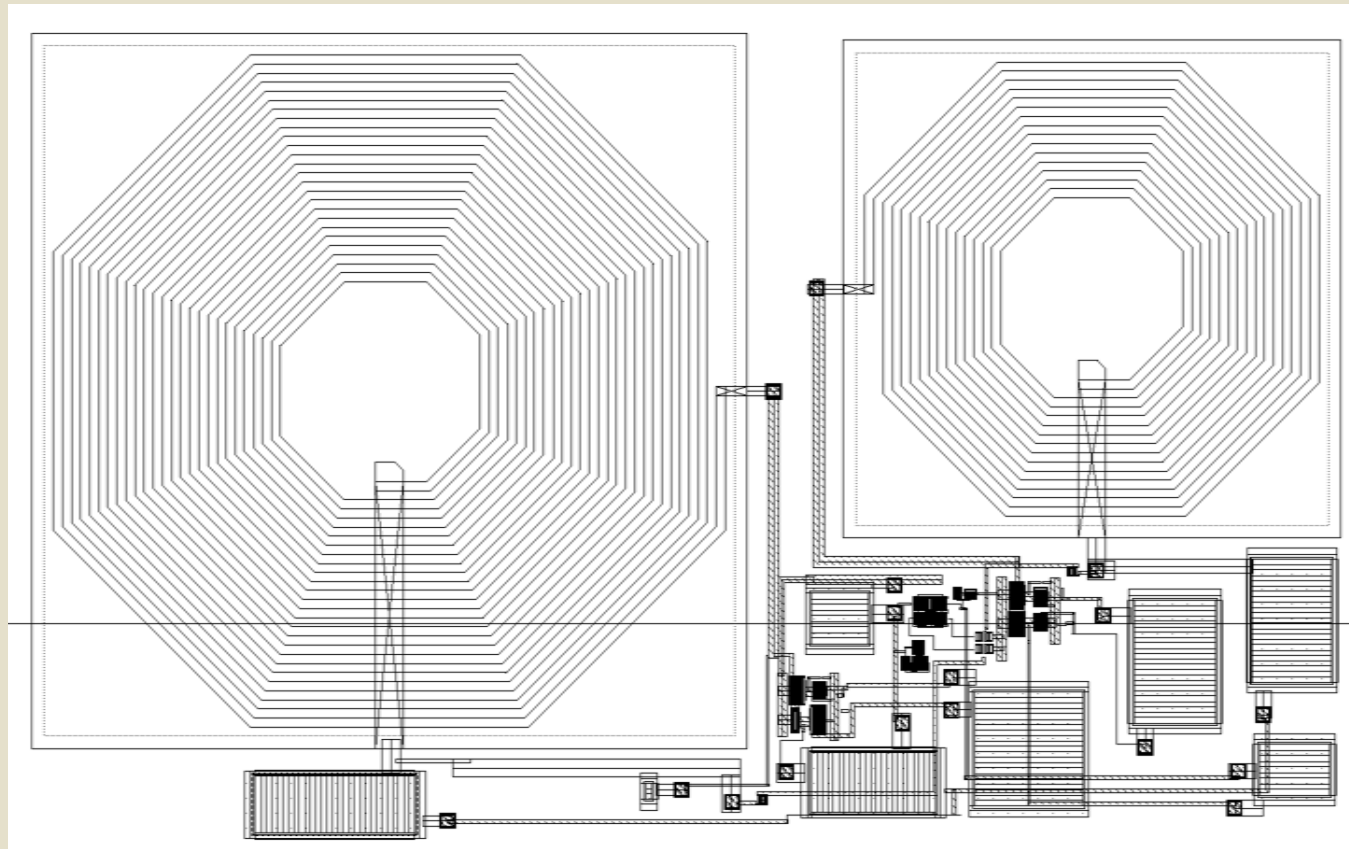

440um

# Results Summary

Parameter	Select GSM-850	Select GSM-1900
Center freq.	906.1 MHz	1888Mhz
S11	-15.0dB	-10.69dB
S21	29.86dB	12.74dB
NF	2.92dB	2.88dB
3dB-BW	85.2MHz	905MHz
P1dB	-0.5dBm	1.995dBm
IIP3	-12.71dBm	-14.0dBm
Power	13.27mW	12.97mW
Area	0.301 mm <sup>2</sup>	

# Summary

- Switched dual band LNA for GSM 850/1900 bands is presented.
- Active inductors can replace passive inductors
  - Reduce unit cost
  - Power and noise disadvantage
- Still needs passive inductor at input port for high Q and reasonable noise figure

Questions?

---

# References

- Active inductor quality factor: Grozing, M.; Pascht, A.; Berroth, M., "A 2.5 V CMOS differential active inductor with tunable L and Q for frequencies up to 5 GHz," *Radio Frequency Integrated Circuits (RFIC) Symposium, 2001. Digest of Papers. 2001 IEEE* , vol., no., pp.271-274, 2001
- "3GPP TS 45.005 V8.4.0," Technical Specification Group GSM/EDGE, Radio Access Network; Radio transmission and reception. Feb 2009.
- R. Ramzan, S. Andersson, J. Dabrowski, and C. Svensson, "A 1.4V 25mW inductorless wideband LNA in 0.13um CMOS," *ISSCC Dig. Tech. Papers*, 2007, pp. 424-613
- D. Shi, N. Behdad, J. Chen, M.P. Flynn, "A 5GHz fully integrated super-regenerative receiver with on-chip slot antenna in 0.13um CMOS," *VLSI Circuits Symposium*, Jun 2008
- Thanachayanont, A.; Payne, A., "VHF CMOS integrated active inductor," *Electronics Letters* , vol.32, no.11, pp.999-1000, 23 May 1996
- Zhuo, W.; de Gyvez, J.P.; Sanchez-Sinencio, E., "Programmable low noise amplifier with active-inductor load," *Circuits and Systems, 1998. ISCAS '98. Proceedings of the 1998 IEEE International Symposium on* , vol.4, no., pp.365-368 vol.4, 31 May-3 Jun 1998